

# EN164: Design of Computing Systems

## Lecture 05: Lab Foundations / Verilog 1

Professor Sherief Reda

<http://scale.engin.brown.edu>


Electrical Sciences and Computer Engineering  
School of Engineering  
Brown University  
Spring 2011



# Introduction to Verilog

- Differences between hard definition language (HDL) and software languages? Concurrency, propagation of time, signal dependency or sensitivity
- Verilog is case sensitive and syntax is similar to C
- Comments are designated by // to the end of a line or by /\* to \*/ across several lines.
- Many online textbooks available from Brown library
  - [Introduction to Logic Synthesis using Verilog HDL](#)
  - [Verilog Digital System Design](#)
  - [Verilog Quickstart](#)
  - [The Verilog Hardware Description Language](#)

# Verilog modules

 

The functionality of each module can be defined with three modeling levels:


1. *Structural or gate level*
2. Dataflow level
3. Behavioral or algorithmic level

Verilog allows different levels of abstraction to be mixed in the same module.
 
# 1. Structural modeling -- Data types: bits


- Nets represent connections between hardware elements. They are continuously driven by output of connected devices. They are declared using the keyword `wire`.

- `wire s1;`
- `wire c1, c2;`
- `wire d=0;`


 
# Modules and ports

```
module FA(A, B, Cin, S, Cout);  
input A, B, Cin;  
output S, Cout;  
...  
endmodule
```



- All port declarations (input, output, inout) are implicitly declared as wire.
- If an output should hold its value, it must be declared as reg

```
module FA(input A, input B, input Cin, output S, output Cout);  
...  
endmodule
```

# Gate level modeling

```
wire Z, Z1, OUT, OUT1, OUT2, IN1, IN2;  
  
and a1(OUT1, IN1, IN2);  
nand na1(OUT2, IN1, IN2);  
xor x1(OUT, OUT1, OUT2);  
not (Z, OUT);  
buf final (Z1, Z);
```

- Essentially describes the topology of a circuit
- All instances are executed concurrently just as in hardware
- Instance name is not necessary
- The first terminal in the list of terminals is an output and the other terminals are inputs
- Not the most interesting modeling technique for our class



# 1 bit full adder example

```


module FA(A, B, Cin, S, Cout);
input A, B, Cin;
output S, Cout;
wire s1, c1, c2;

xor g1(s1, A, B);
xor g2(S, s1, Cin);
and g3(c1, s1, Cin);
and g4(c2, A, B);
or g5(Cout, c1, c2);
endmodule

```

  

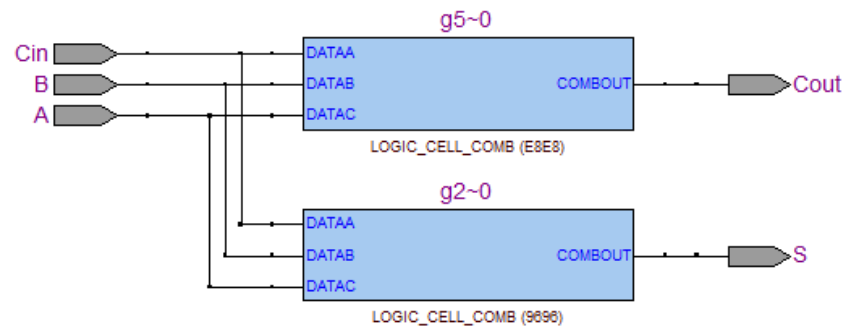[from Tools → Netlist Viewers → RTL Viewer]



[from Tools → Netlist Viewers → after technology mapping]


# Data types: vectors

- A net or register can be declared as *vectors*. Example of declarations:
  - `wire a;`
  - `wire [7:0] bus;`
  - `wire [31:0] busA, busB, busC;`
- It is possible to access bits or parts of vectors
  - `busA[7]`
  - `bus[2:0]`
  - `virt_addr[0:2]`



# Specifying values for wires and variables

- Number specification.

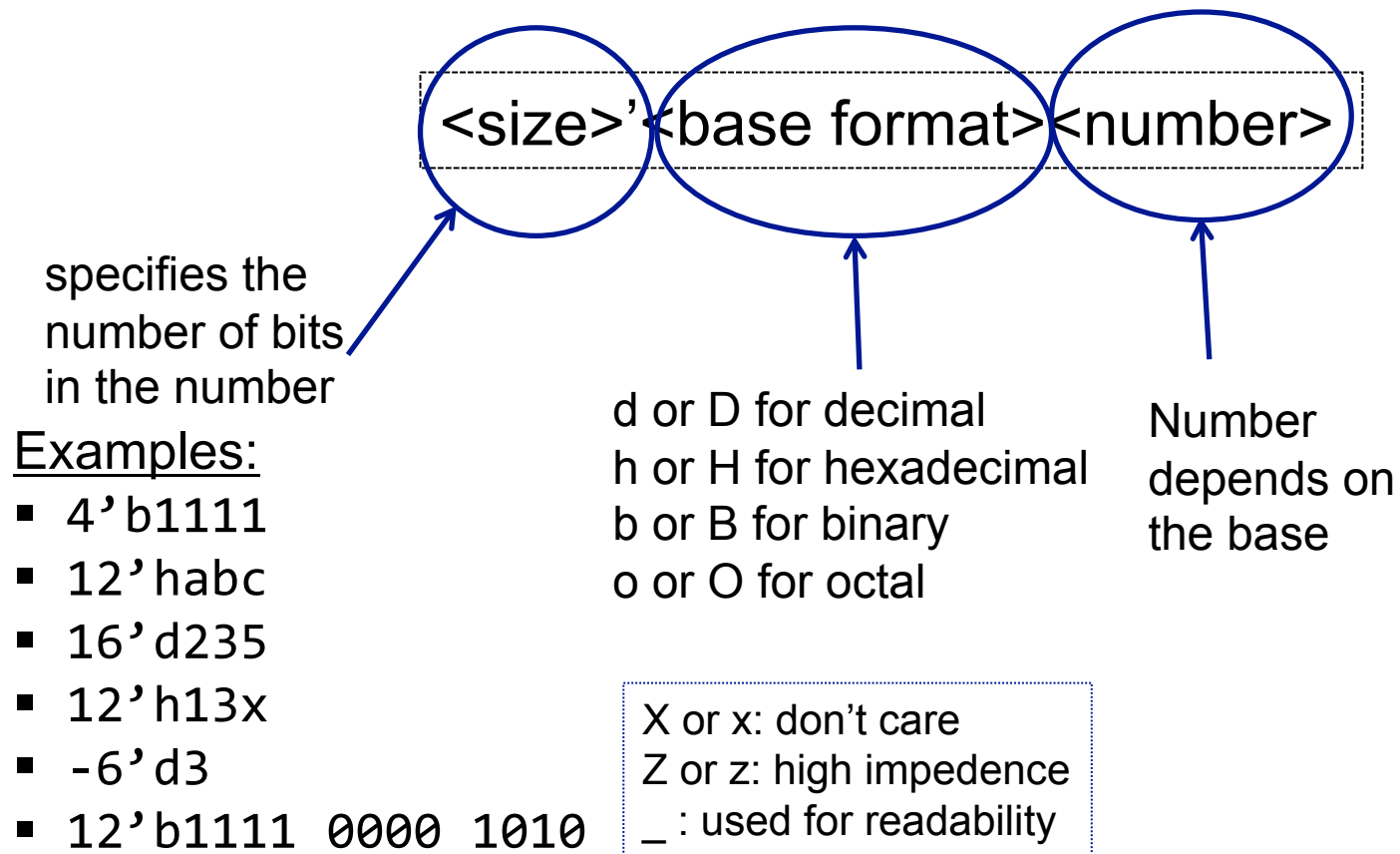

# Modules with input / output vectors


```
module fulladd4(output reg[3:0] sum,  
               output reg c_out,  
               input [3:0] a, b,  
               input c_in);  
...  
...  
endmodule
```

**OR**

```
module fulladd4(sum, c_out, a, b, input c_in);  
output reg [3:0] sum  
output reg c_out;  
input [3:0] a, b;  
input c_in;  
...  
...  
endmodule
```
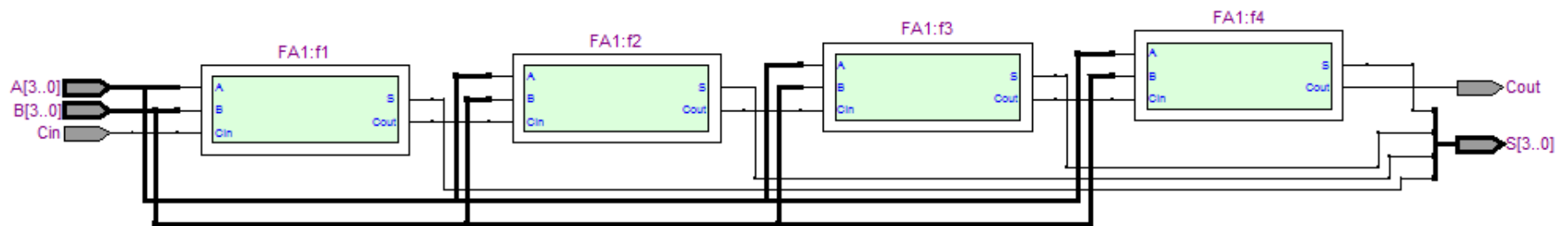
# Module instantiation

```
module fulladd4(A, B, Cin, S, Cout);  
input [3:0] A, B;  
input Cin;  
output [3:0] S;  
output Cout;  
wire C1, C2, C3;  
  
FA f1(A[0], B[0], Cin, S[0], C1);  
FA f2(A[1], B[1], C1, S[1], C2);  
FA f3(A[2], B[2], C2, S[2], C3);  
FA f4(A[3], B[3], C3, S[3], Cout);  
endmodule
```



[from Tools → Netlist Viewers → RTL Viewer]

# Alternative form of module instantiation

```
module FA(A, B, Cin, S, Cout);  
input A, B, Cin;  
output S, Cout;  
...  
endmodule
```

```
wire a1, a2, a3, a4, a5
```

```
FA f1(a1, a2, a3, a4, a5);
```

**OR**

```
FA1 f1(.Cout(a5), .S(a4), .B(a2), .A(a1), .C_IN(a3));
```

# Instantiation an array of gates

```
wire [7:0] OUT, IN1, IN2;

// array of gates instantiations
nand n_gate [7:0] (OUT, IN1, IN2);

// which is equivalent to the following
nand n_gate0 (OUT[0], IN1[0], IN2[0]);
nand n_gate1 (OUT[1], IN1[1], IN2[1]);
nand n_gate2 (OUT[2], IN1[2], IN2[2]);
nand n_gate3 (OUT[3], IN1[3], IN2[3]);
nand n_gate4 (OUT[4], IN1[4], IN2[4]);
nand n_gate5 (OUT[5], IN1[5], IN2[5]);
nand n_gate6 (OUT[6], IN1[6], IN2[6]);
nand n_gate7 (OUT[7], IN1[7], IN2[7]);
```

## 2. Dataflow modeling

- Module is designed by specifying the data flow, where the designer is aware of how data flows between hardware registers and how the data is processed in the design
- The continuous assignment is one of the main constructs used in dataflow modeling
  - `assign out = i1 & i2;`
  - `assign addr[15:0] = addr1[15:0] ^ addr2[15:0];`
  - `assign {c_out, sum[3:0]}=a[3:0]+b[3:0]+c_in;`
- A continuous assignment is always active and the assignment expression is evaluated as soon as one of the right-hand-side variables change
- Assign statements describe hardware that operates concurrently – ordering does not matter
- Left-hand side must be a scalar or vector net. Right-hand side operands can be wires, (registers, integers, and real)

# Operator types in dataflow expressions

- Operators are similar to C except that there are no ++ or –
- Arithmetic: \*, /, +, -, % and \*\*
- Logical: !, && and ||
- Relational: >, <, >= and <=
- Equality: ==, !=, === and !==
- Bitwise: ~, &, |, ^ and ^~
- Reduction: &, ~&, |, ~|, ^ and ^~
- Shift: << and >>
- Concatenation: { }
- Replication: {{}}
- Conditional: ?: