

EN164: Design of Computing Systems

Lecture 12: Processor / Single-Cycle Design 1

Professor Sherief Reda

<http://scale.engin.brown.edu>

Electrical Sciences and Computer Engineering
School of Engineering
Brown University
Spring 2011



[material from Patterson & Hennessy, 4th ed and Harris 1st ed]

Processor organization (microarchitecture)

- Multiple implementations for a single architecture:
 - Single-cycle
 - Each instruction executes in a single cycle
 - Multi-cycle
 - Each instruction is broken up into a series of shorter steps
 - Pipelined
 - Each instruction is broken up into a series of steps
 - Multiple instructions execute at once.


Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

Introduction

- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware
- We will examine two MIPS implementations
 - A simplified version
 - A more realistic pipelined version
- Simple subset, shows most aspects
 - Memory reference: lw, sw
 - Arithmetic/logical: add, sub, and, or, slt
 - Control transfer: beq, j


Architectural state

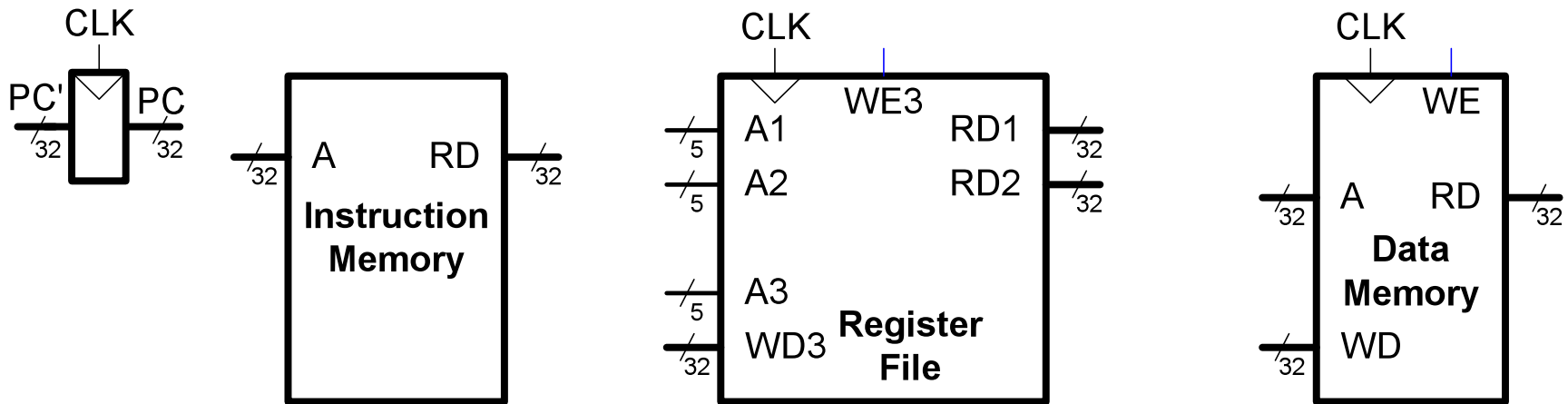- Determines everything about a processor:
 - PC
 - 32 registers
 - Memory




Single-Cycle MIPS Processor

- Datapath
- Control

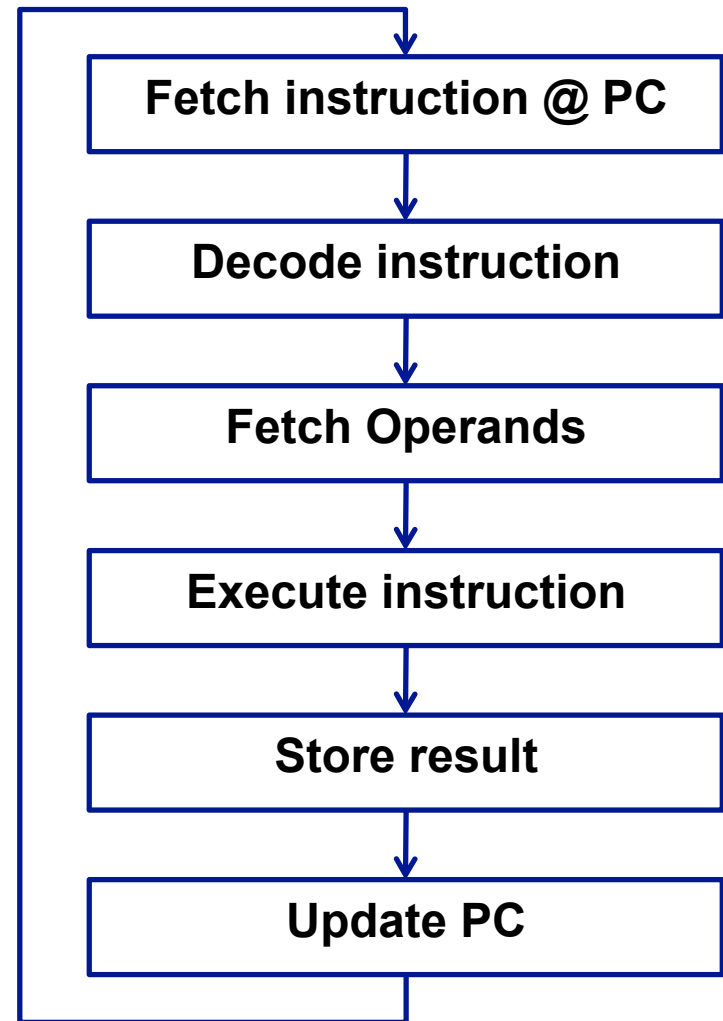


Single-Cycle Datapath: l_w fetch

 - First consider executing l_w
- **STEP 1: Fetch instruction**




Single-Cycle Datapath: l_w register read

 - **STEP 2:** Read source operands from register file




Single-Cycle Datapath: l_w immediate

- **STEP 3:** Sign-extend the immediate

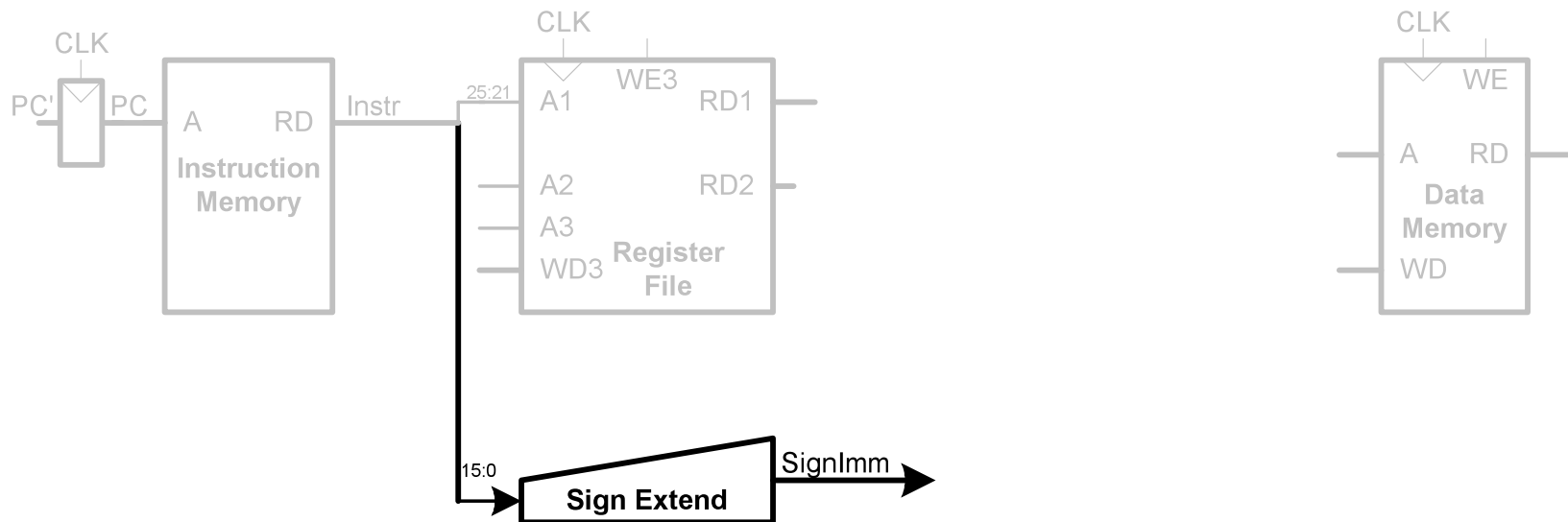


Single-Cycle Datapath: l_w address

- **STEP 4:** Compute the memory address

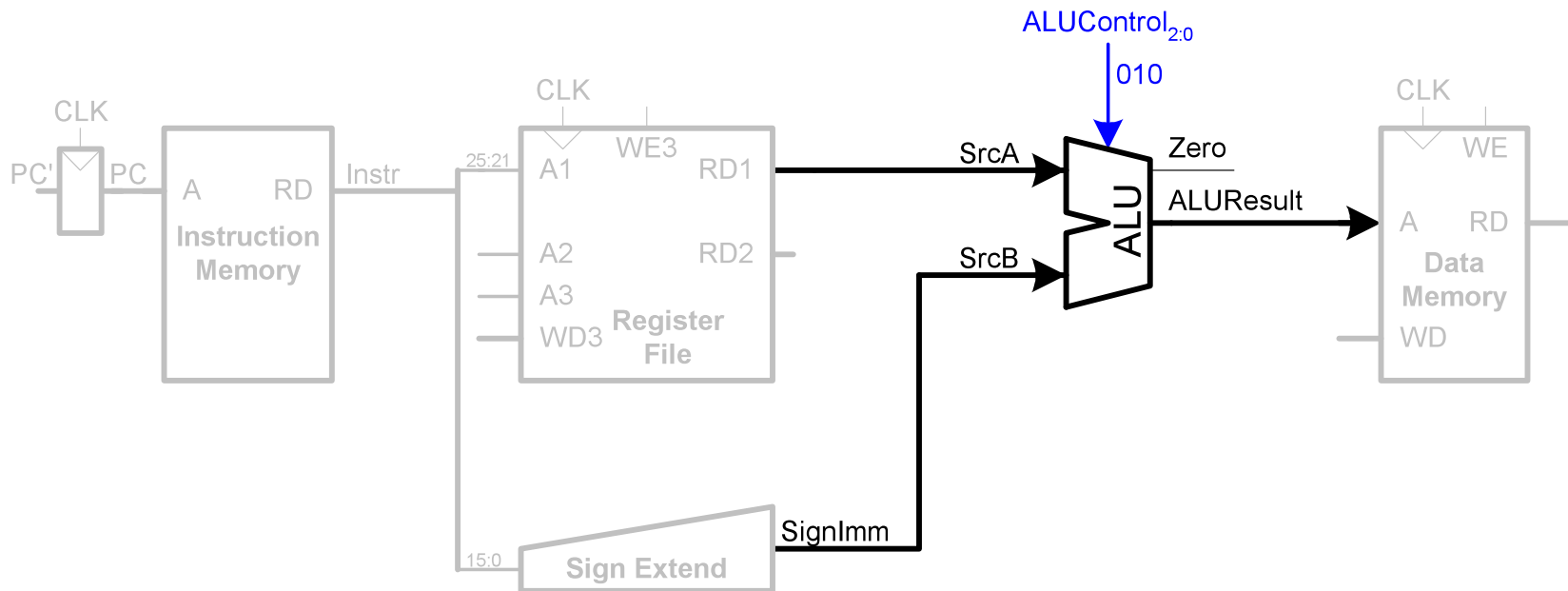

Single-Cycle Datapath: \perp_W memory read

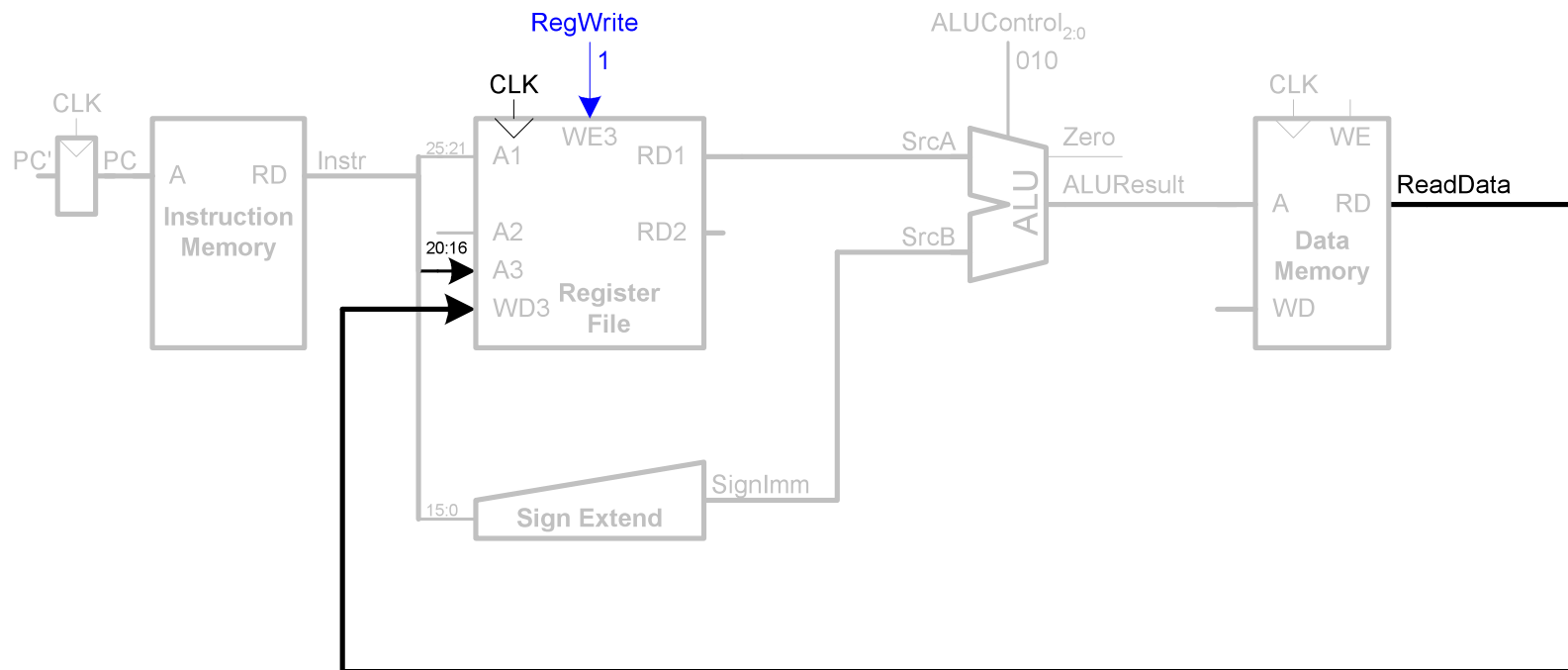- **STEP 5:** Read data from memory and write it back to register file



Single-Cycle Datapath: l_w PC increment

- **STEP 6:** Determine the address of the next instruction

