

# ENGN1640: Design of Computing Systems

## Topic 04: Single-Cycle Processor Design

Professor Sherief Reda

<http://scale.engin.brown.edu>

Electrical Sciences and Computer Engineering

School of Engineering

Brown University

Spring 2016



[ material from Harris ]

# Processor organization (microarchitecture)

- Multiple implementations for a single architecture:
  - Single-cycle
    - Each instruction executes in a single cycle
  - Multi-cycle
    - Each instruction is broken up into a series of shorter steps
  - Pipelined
    - Each instruction is broken up into a series of steps
    - Multiple instructions execute at once.
  - Superscalar
    - Multiple instructions fetched, decoded and executed simultaneously.


Application Software	programs
Operating Systems	device drivers
Architecture	instructions registers
Micro-architecture	datapaths controllers
Logic	adders memories
Digital Circuits	AND gates NOT gates
Analog Circuits	amplifiers filters
Devices	transistors diodes
Physics	electrons

# Introduction

- CPU performance factors
  - Instruction count
    - Determined by ISA and compiler
  - CPI and Cycle time
    - Determined by CPU hardware
- We will examine a number of ARM implementations
  - A simplified single-cycle version
  - A more realistic pipelined version
- Simple subset, shows most aspects
  - Memory reference: **LDR, STR**
  - Arithmetic/logical: **ADD, SUB, AND, ORR**
  - Control transfer: **B**
- Will not implement in lab post-index, pre-index or shifted operands.
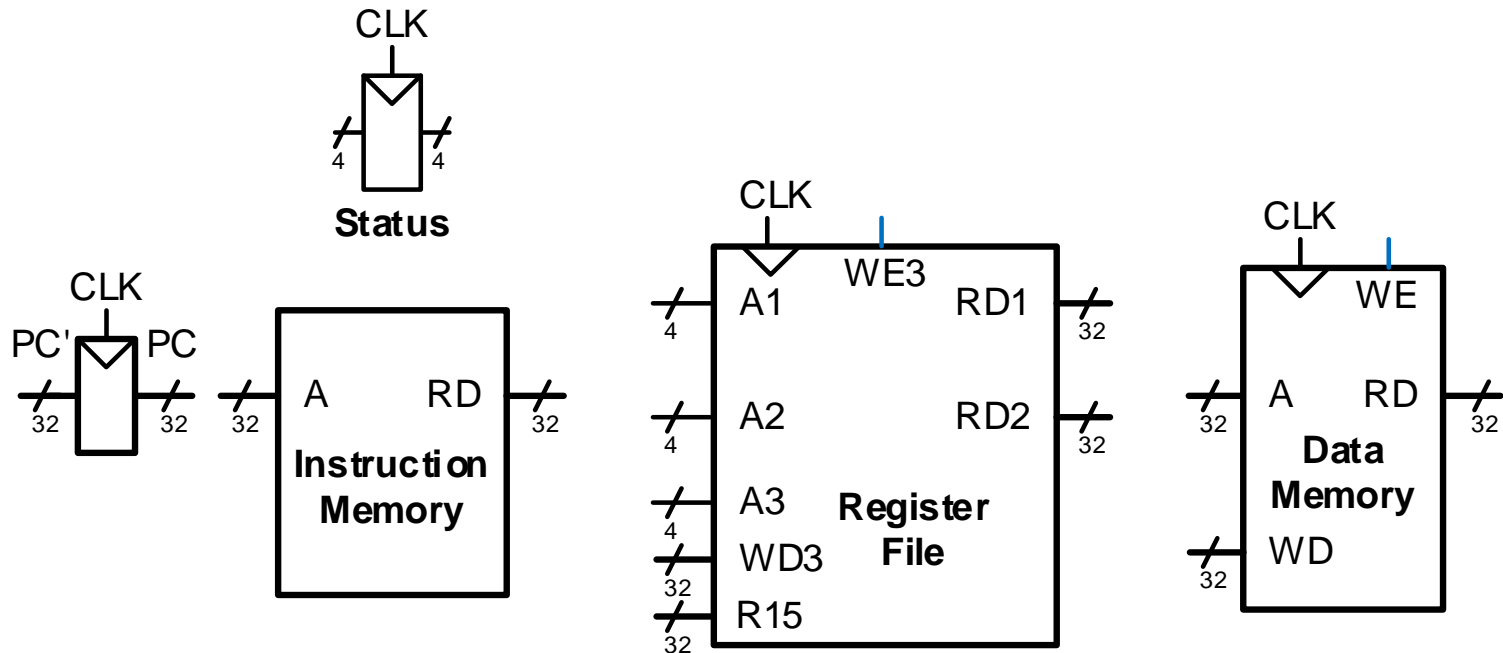
# Architectural state

- Determines everything about a processor:
  - PC
  - 16 registers
  - Memory



# Single-Cycle ARM Processor



- Datapath
- Control

**Datapath:** start with LDR instruction

- **Example:**


LDR R1, [R2, #5]

LDR Rd, [Rn, imm12]

 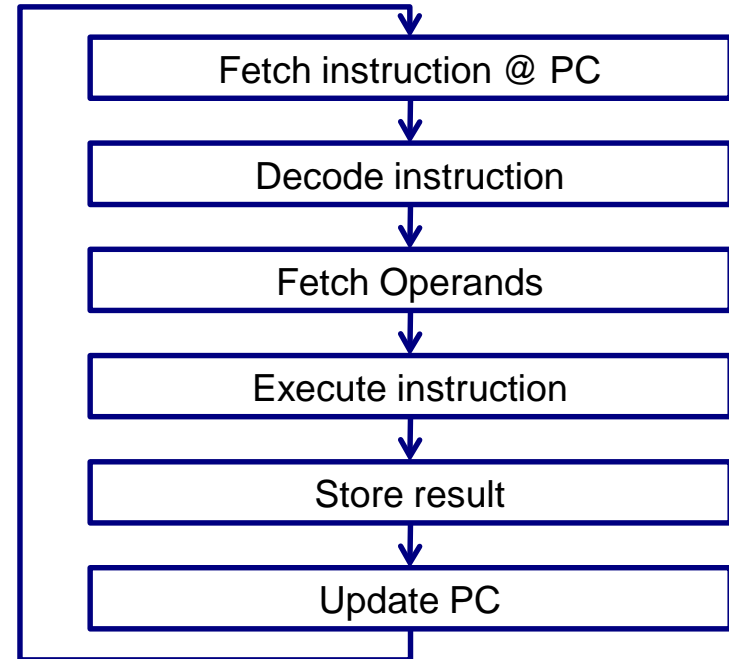



# Single-Cycle Datapath: LDR fetch

- **STEP 1:** Fetch instruction

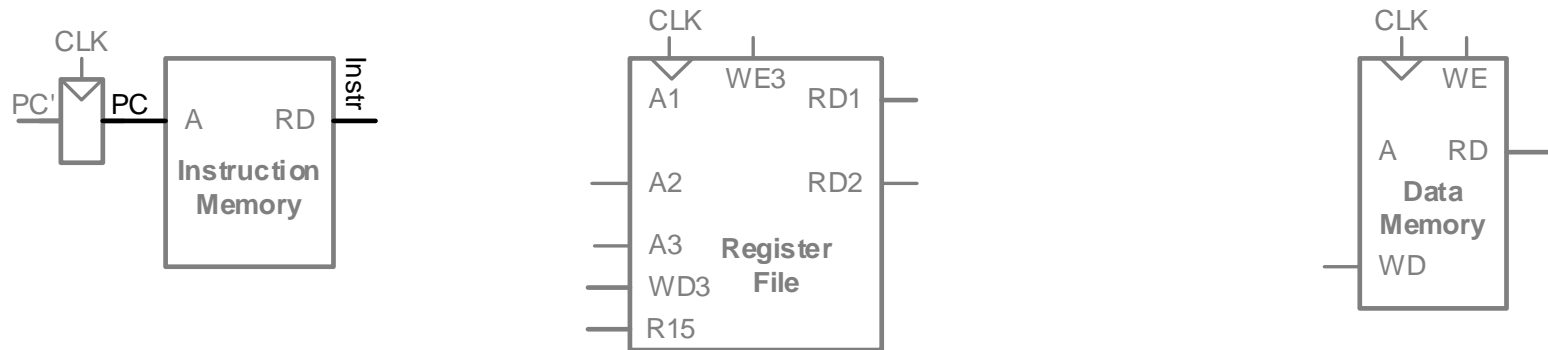

# Single-Cycle Datapath: LDR register read

## STEP 2: Read source operands from RF

 
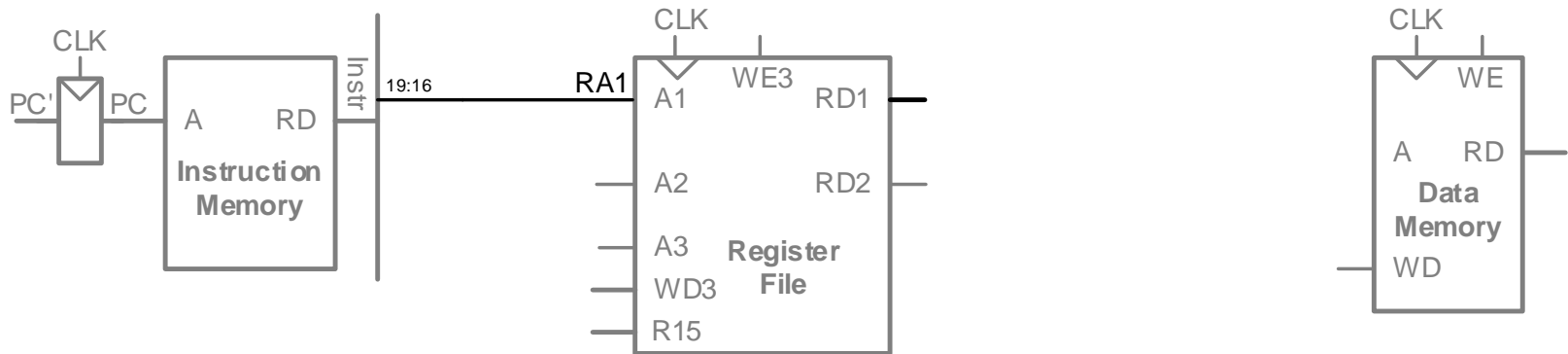








# Single-Cycle Datapath: LDR address

## STEP 4: Compute the memory address

 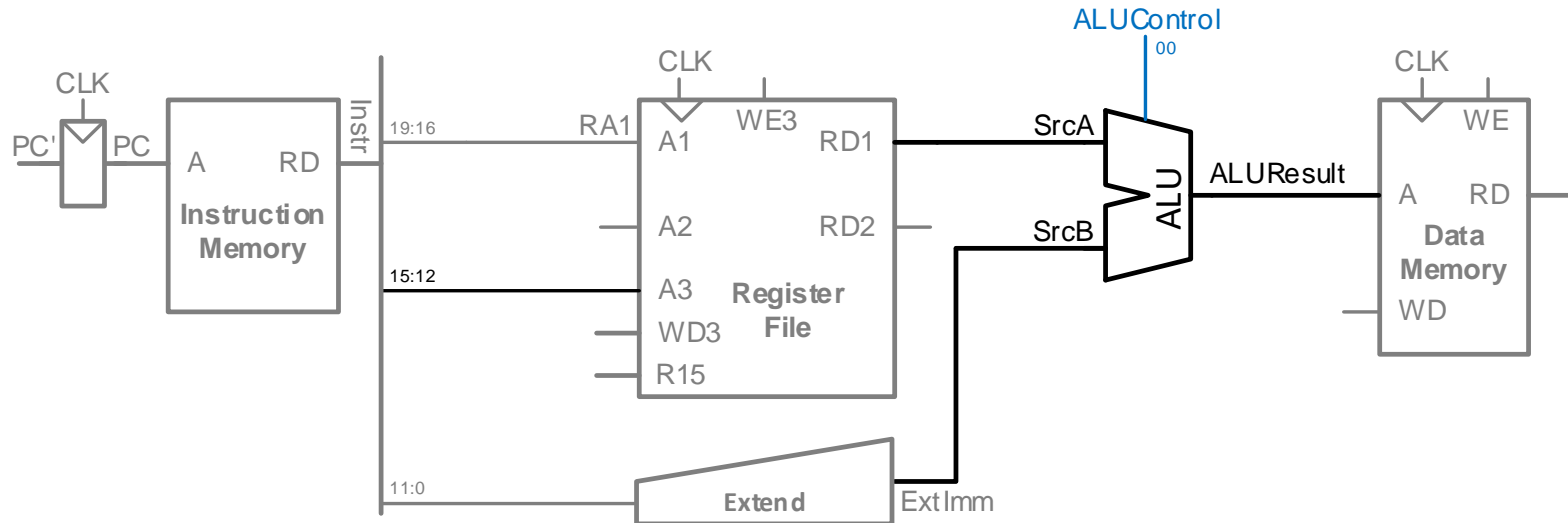

 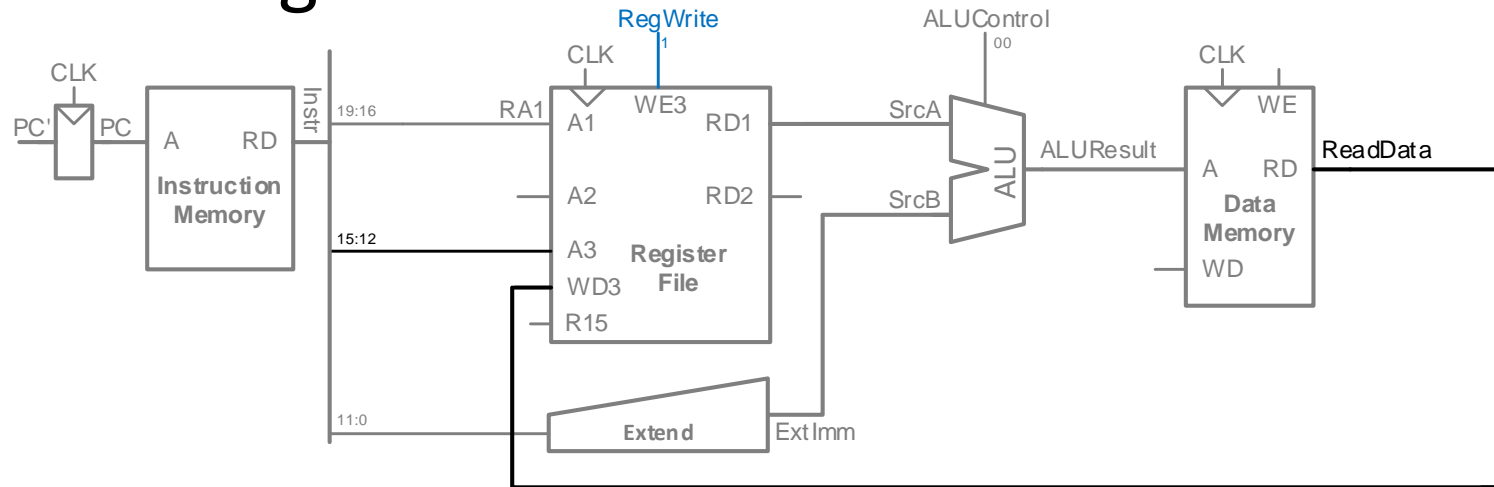
# Single-Cycle Datapath: LDR memory read

**STEP 5:** Read data from memory and write it back to register file



# Single-Cycle Datapath: LDR PC increment

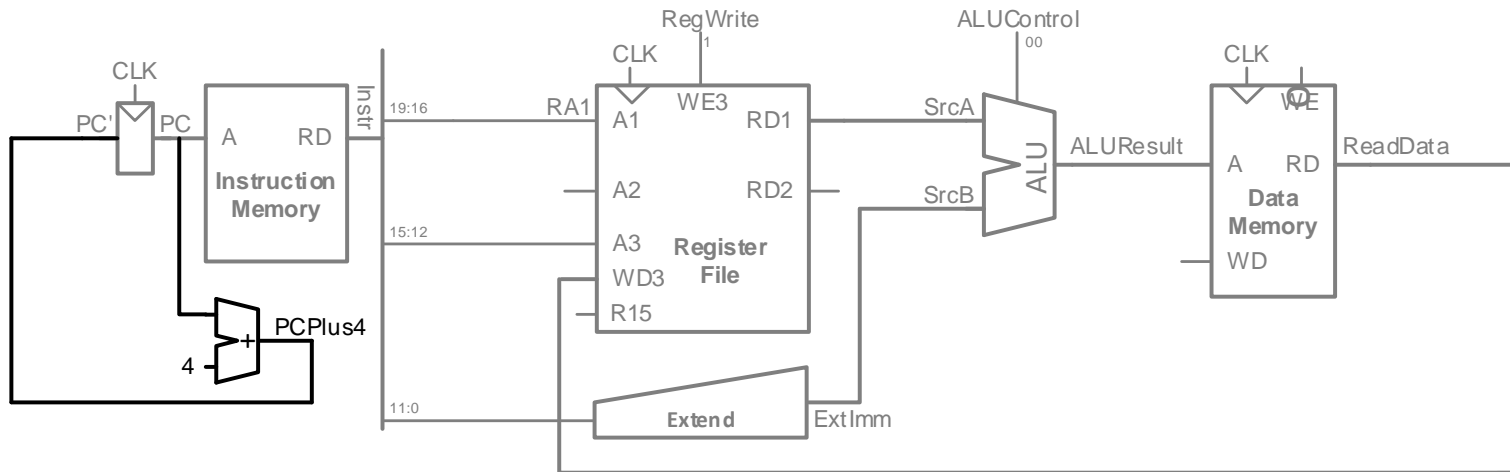
## STEP 6: Determine address of next instruction


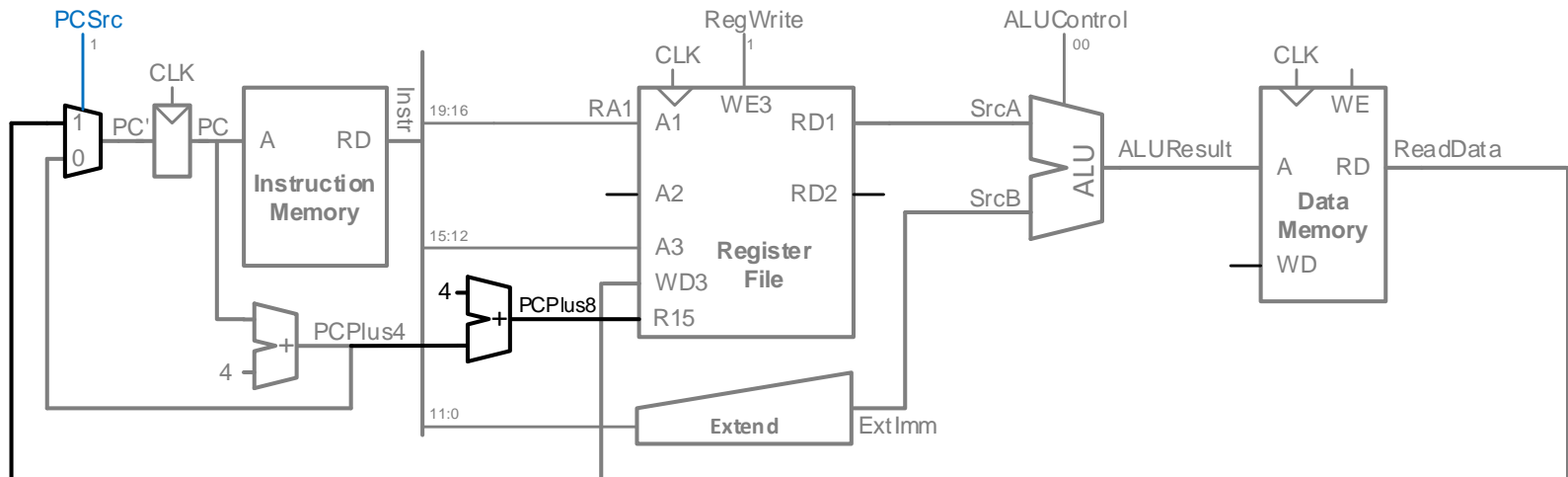
# Single-Cycle Datapath: Access to PC

PC can be source/destination of instruction



- **Source:** R15 must be available in Register File
  - **PC** is read as the current **PC plus 8**
- **Destination:** Be able to write result to PC



# Single-Cycle Datapath: STR

## Expand datapath to handle STR:


- Write data in Rd to memory

 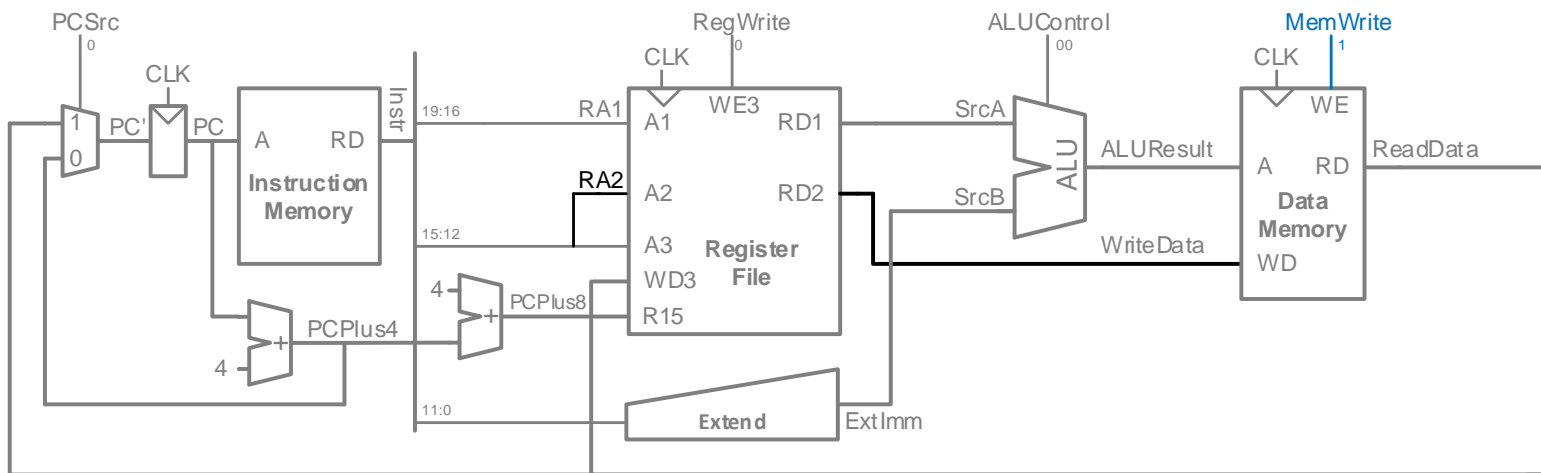


# Single-Cycle Datapath: data processing
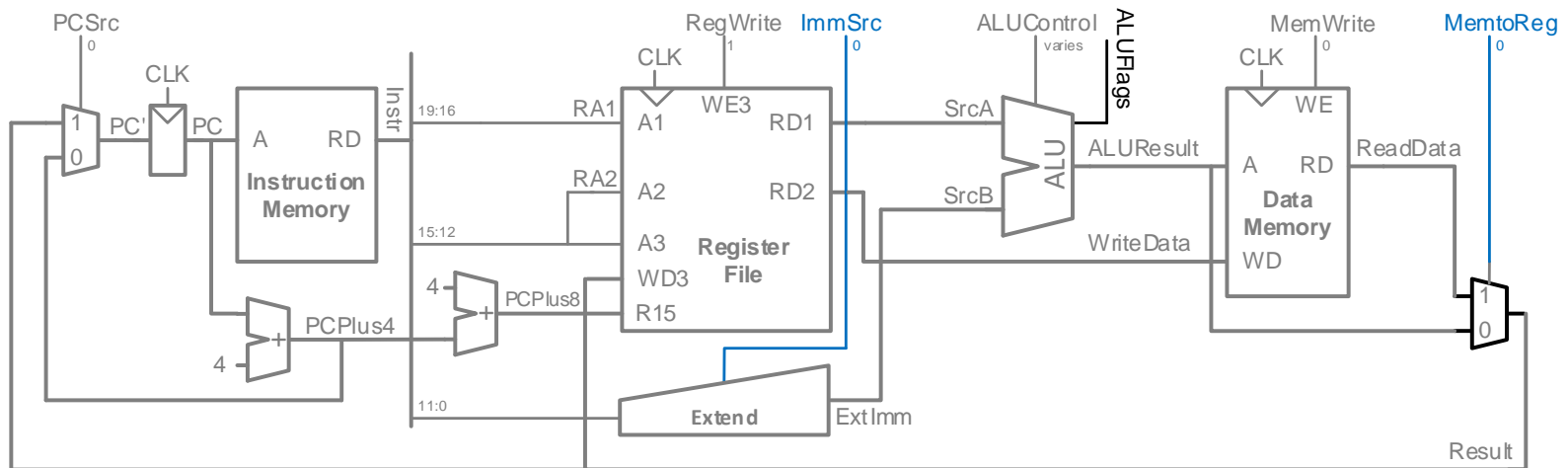
## With **immediate Src2**:

- Read from  $R_n$  and  $Imm8$  ( $ImmSrc$  chooses the zero-extended  $Imm8$  instead of  $Imm12$ )
- Write  $ALUResult$  to register file
- Write to  $R_d$




**ADD  $R_d$ ,  $R_n$ ,  $imm8$**

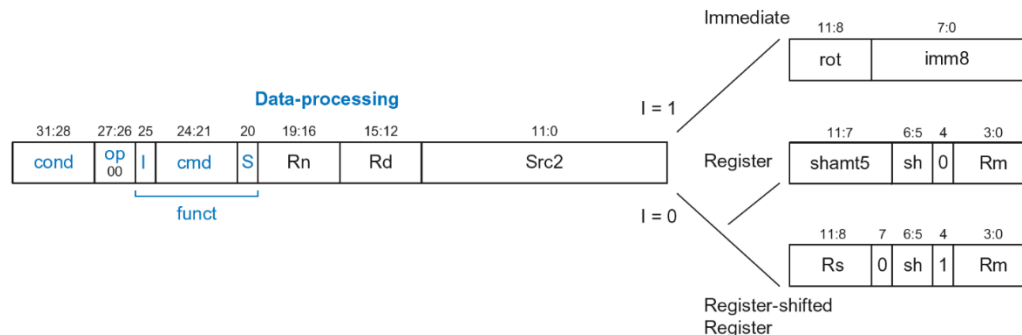


# Single-Cycle Datapath: data processing
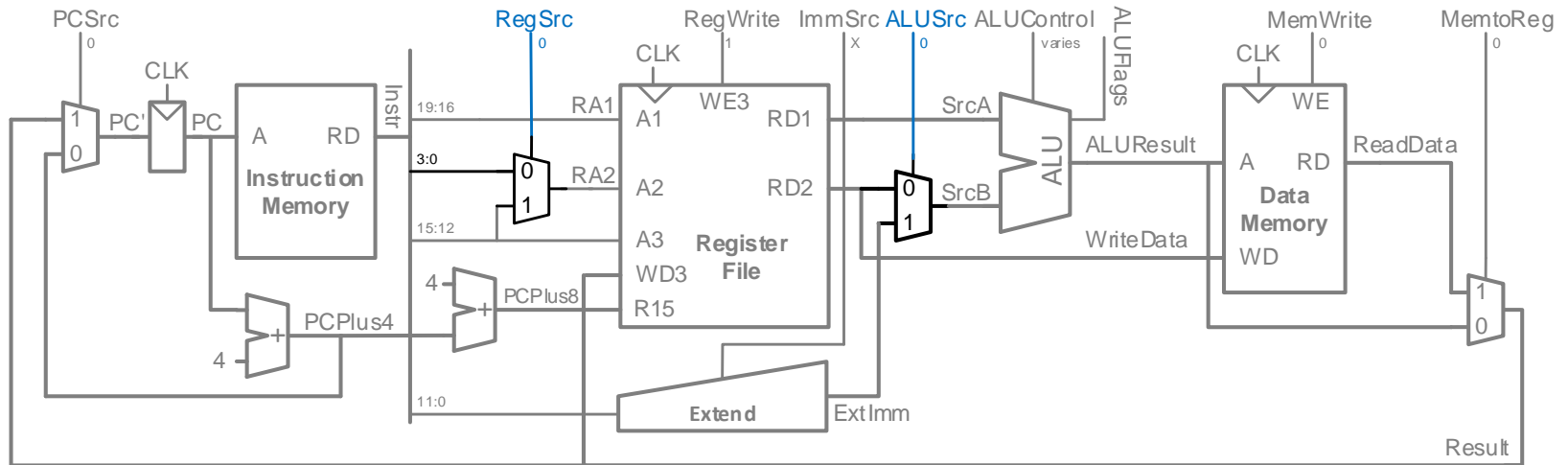
## With register Src2:

- Read from Rn and Rm (instead of Imm8 )
- Write *ALUResult* to register file
- Write to Rd



## ADD Rd, Rn, Rm

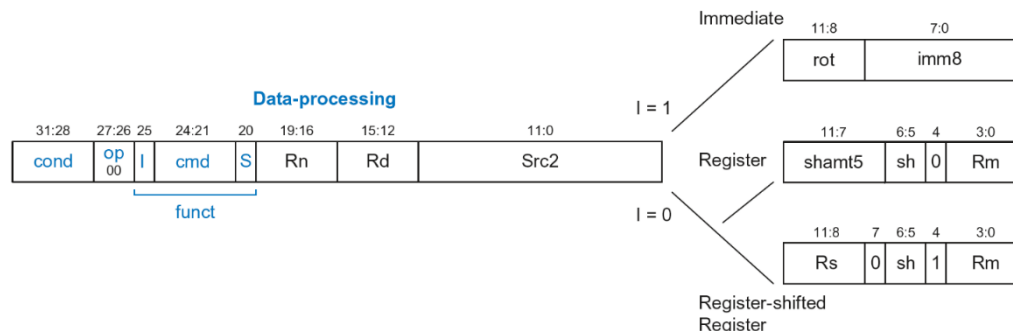












# Single-Cycle ARM processor

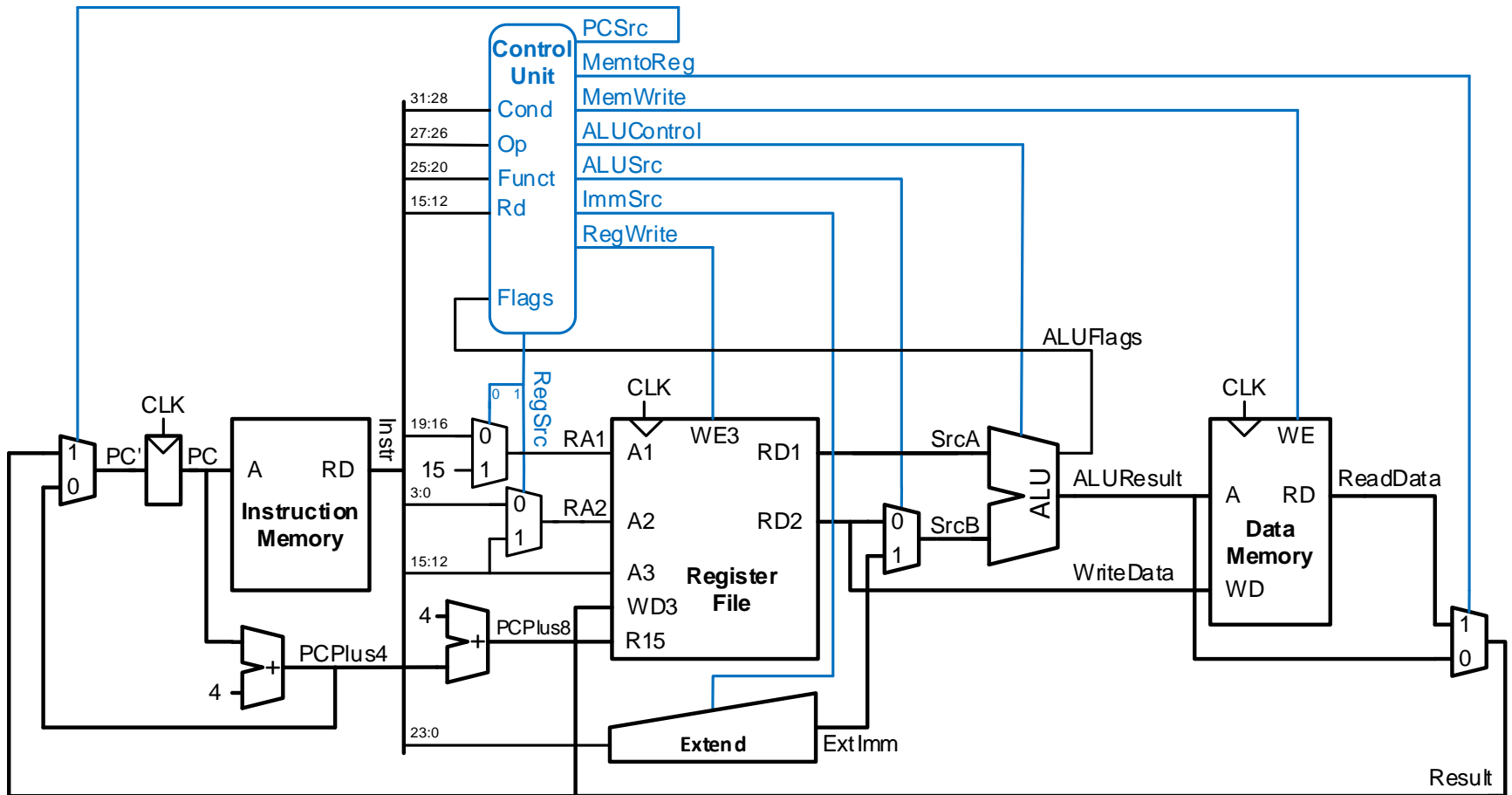

# Single-Cycle Control


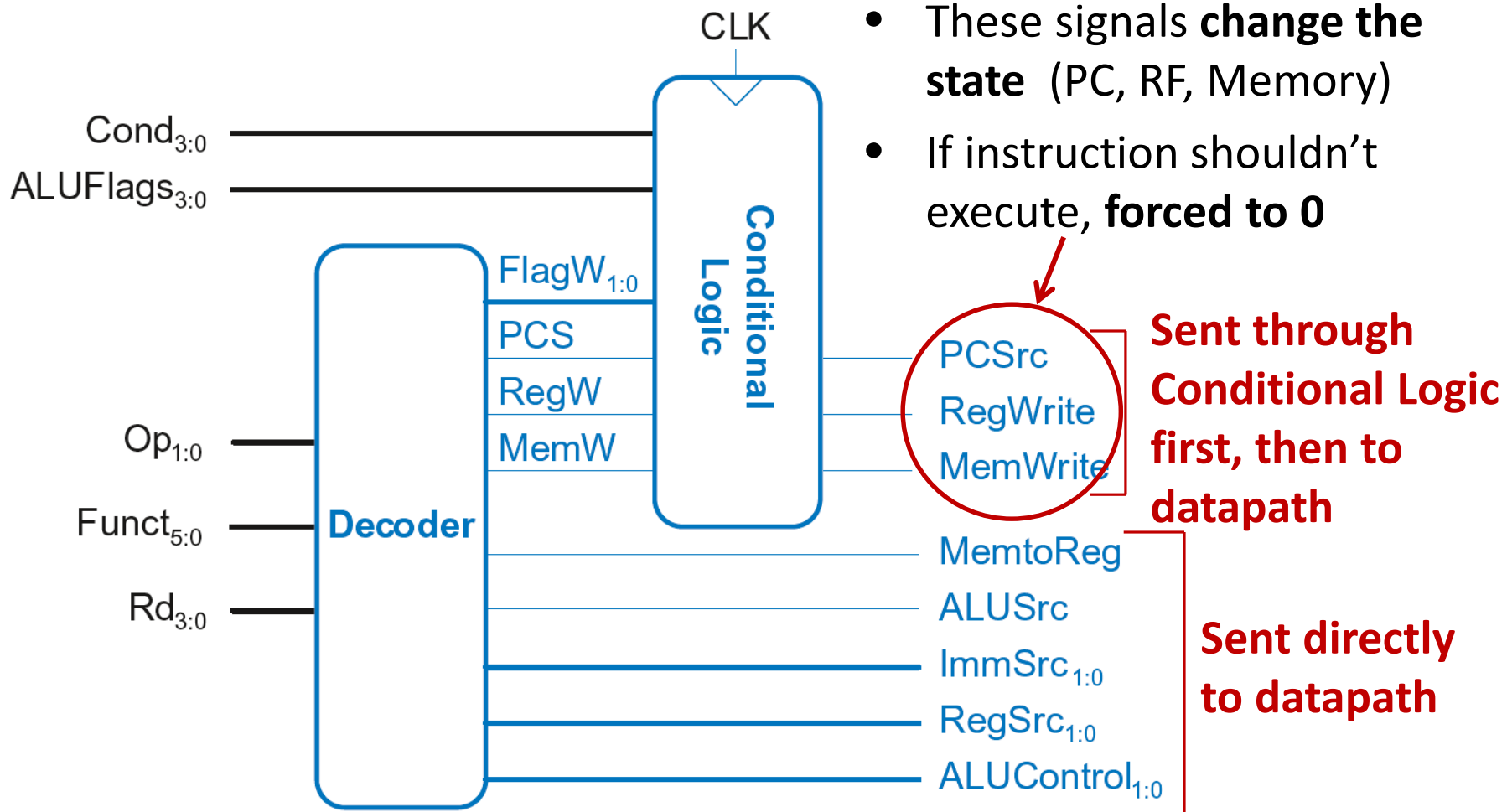


# Single-Cycle control


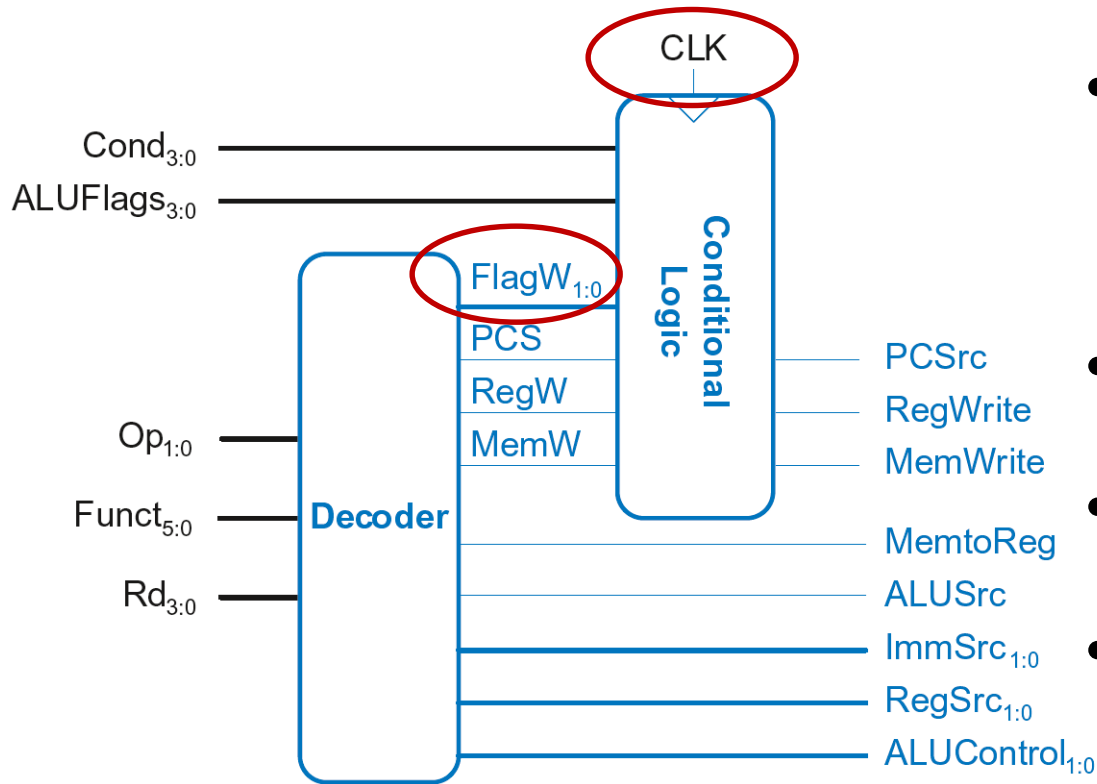


- **$FlagW_{1:0}$** : Flag Write signal, asserted when  $ALUFlags$  should be saved (i.e., on instruction with  $S=1$ )
- ADD, SUB update all flags (**NZCV**)
- AND, ORR only update **NZ** flags
- So, two bits needed:
  - $FlagW_1 = 1$** : NZ saved ( $ALUFlags_{3:2}$  saved)
  - $FlagW_0 = 1$** : CV saved ( $ALUFlags_{1:0}$  saved)

 
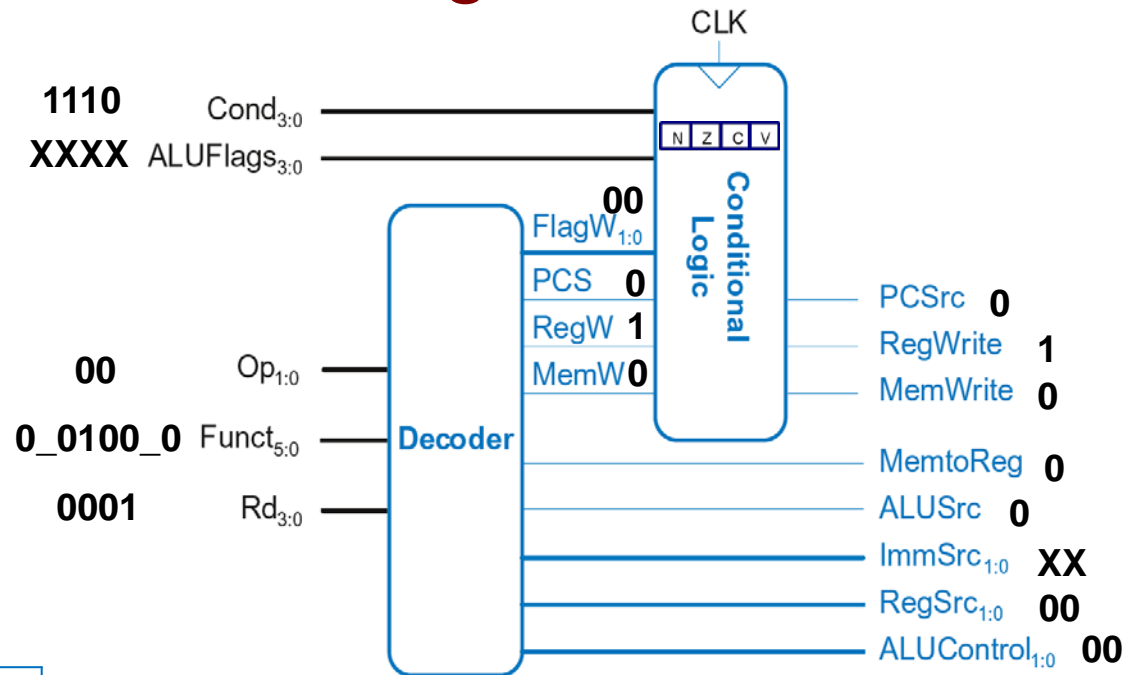
# Example of control logic: ADD R1, R2, R3


 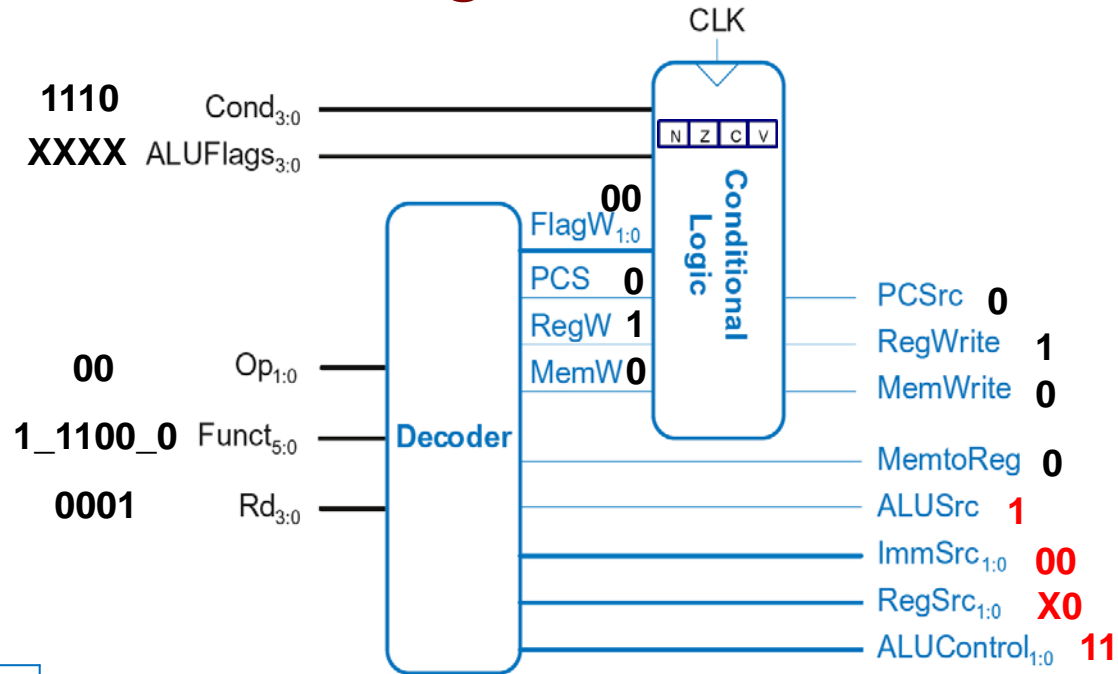
# Example of control logic: ORR R1, R2, #F0



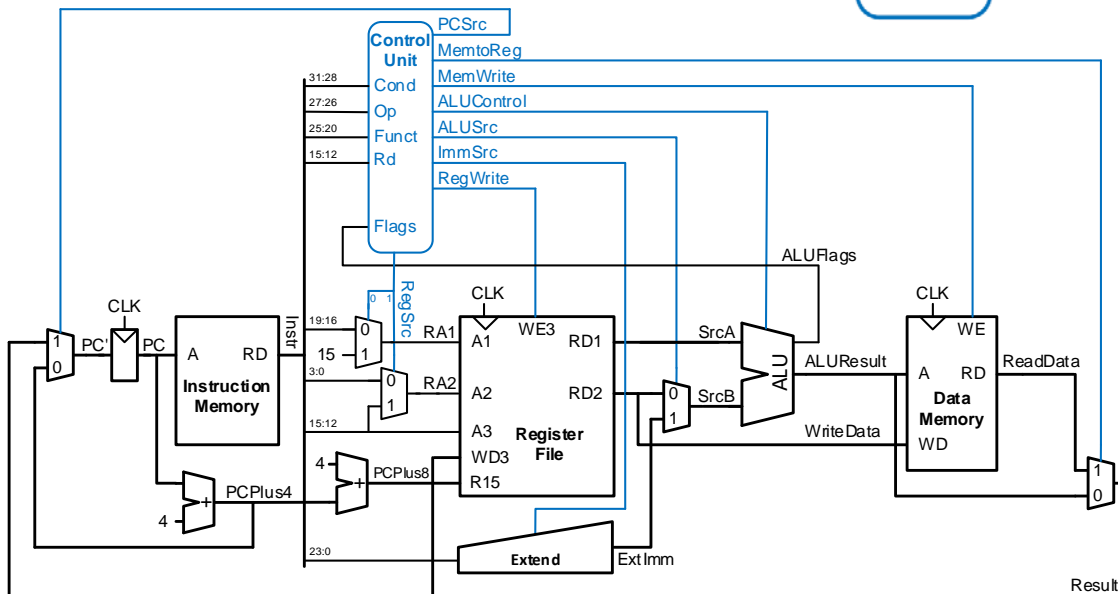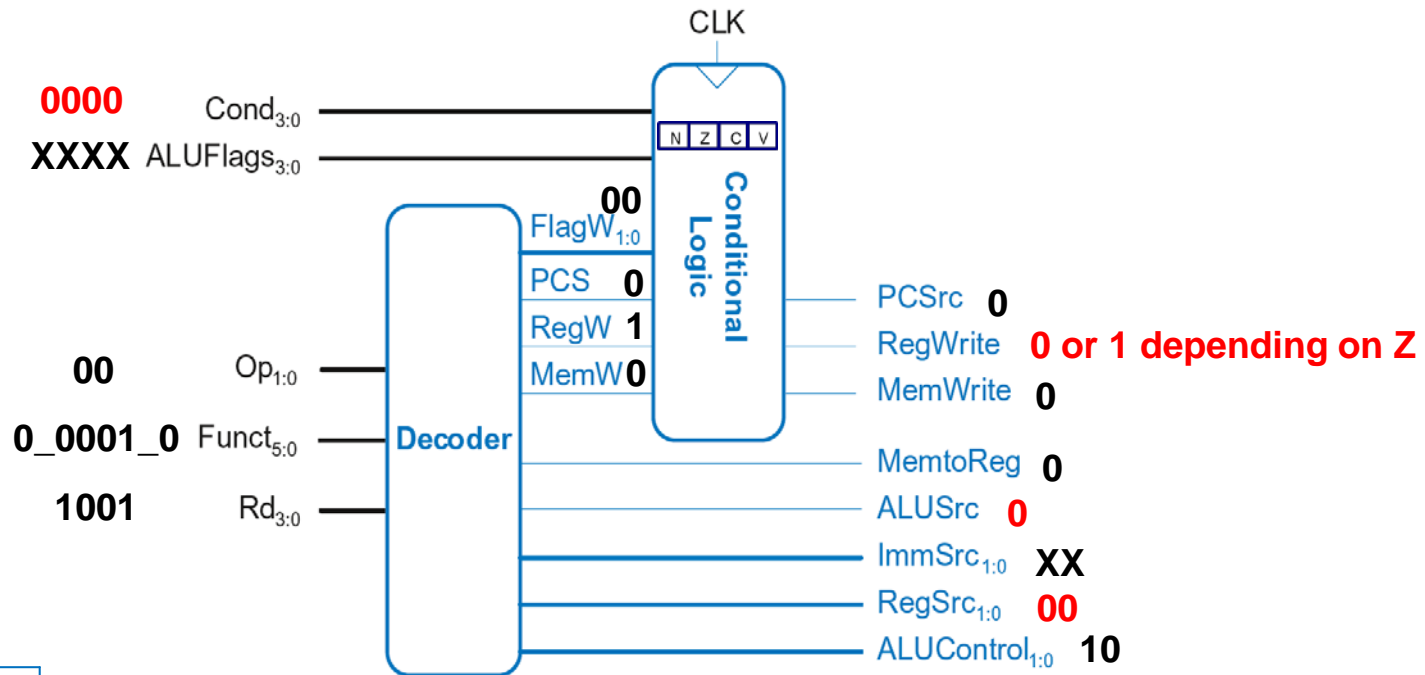
# Example of control logic: ANDEQ R5, R6, R7







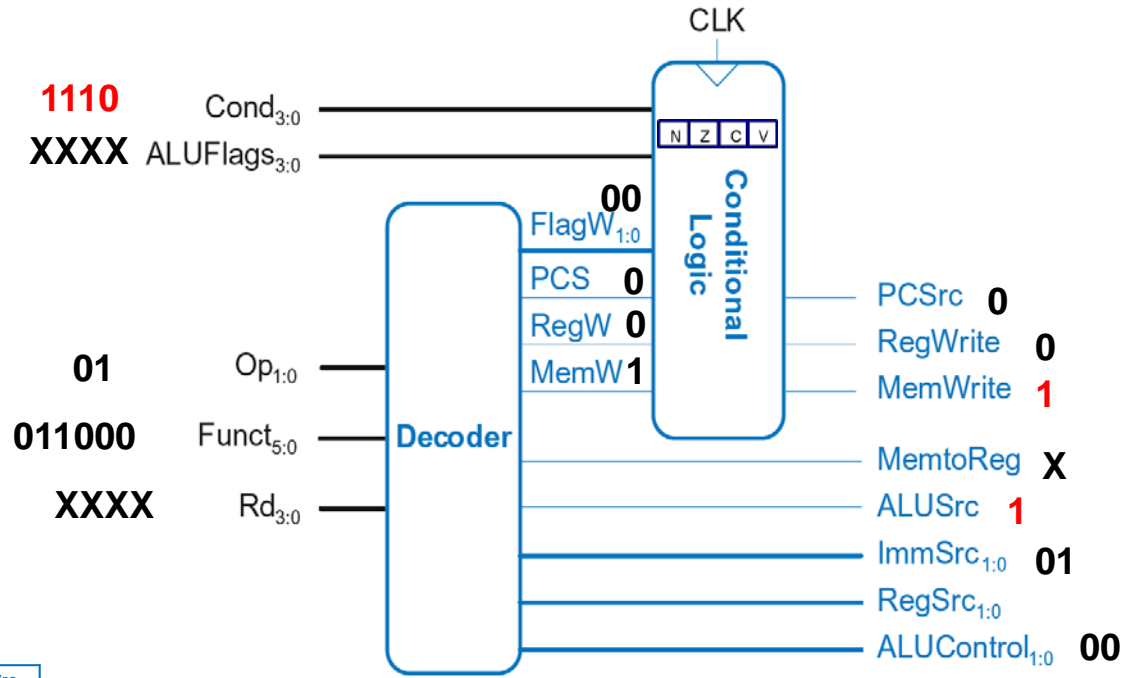
# Example of control logic: STR R11, [R5, #8]





10

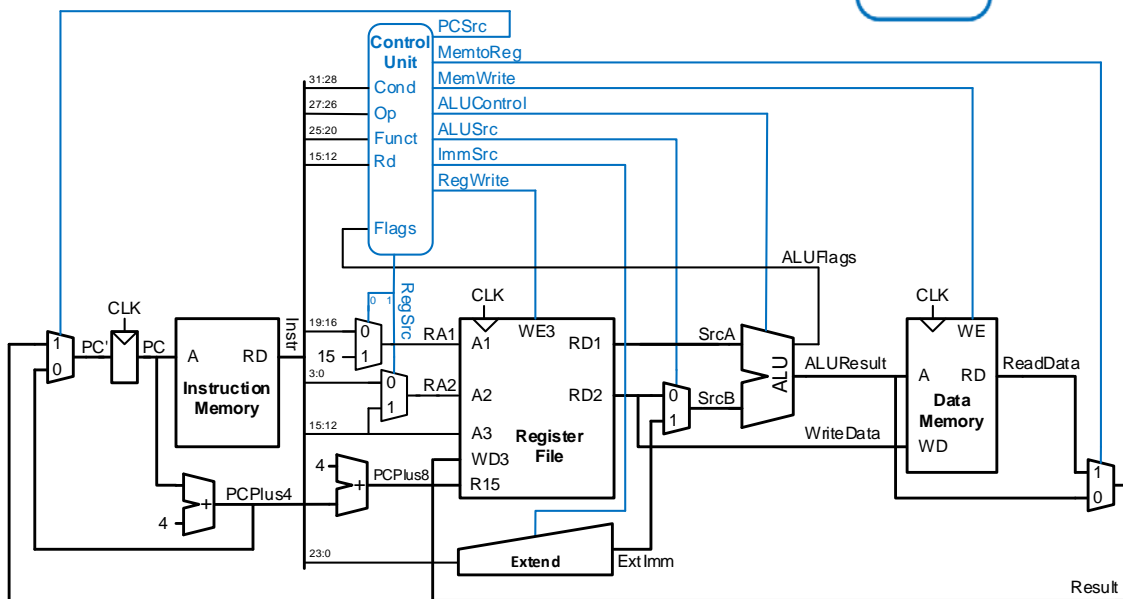



# Example of control logic: BNE THERE

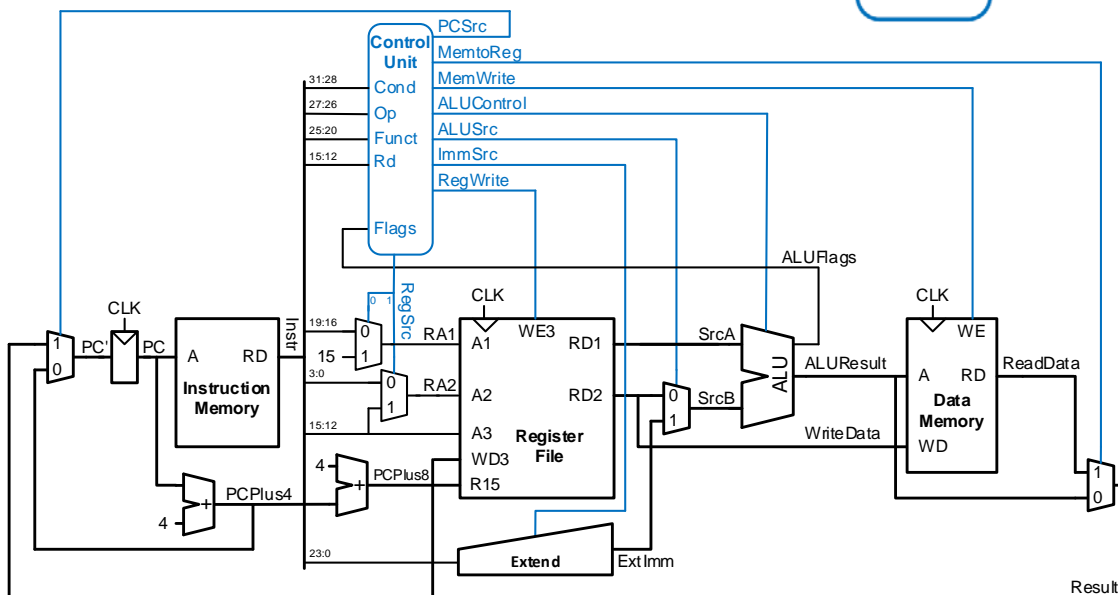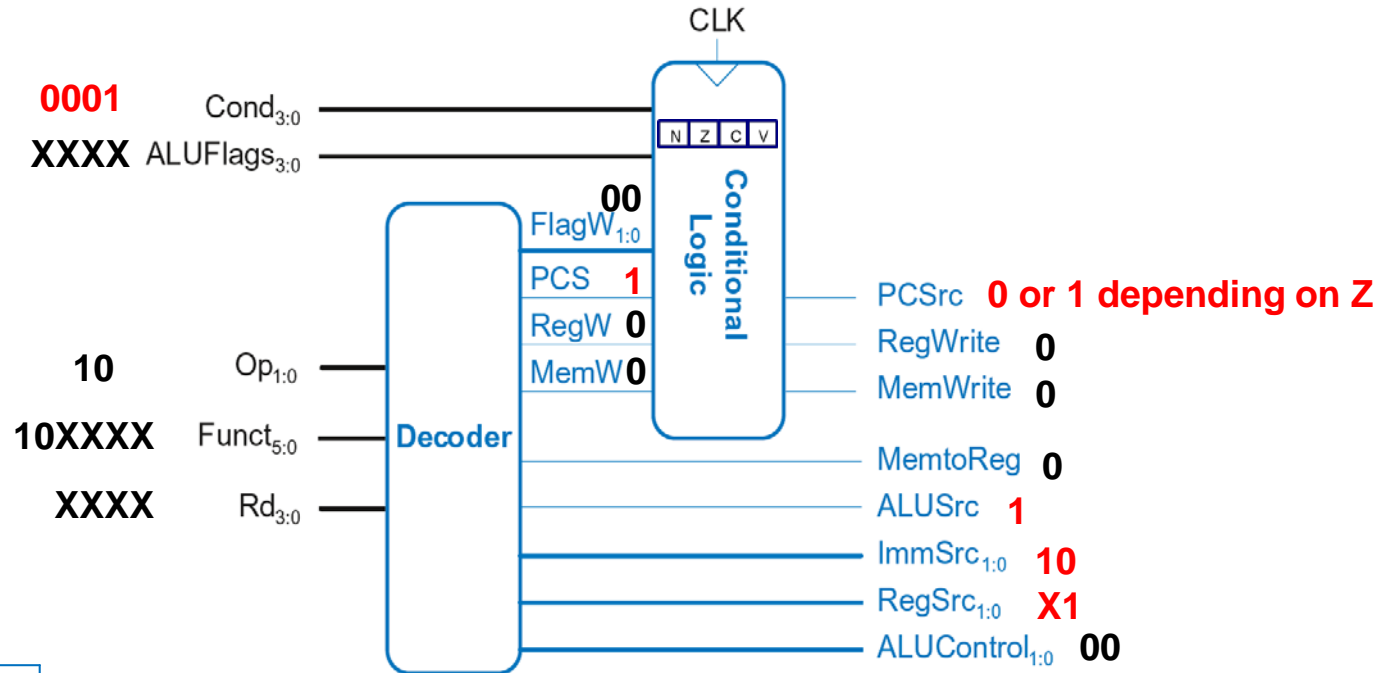


# Example of control logic: CMP R1, R2

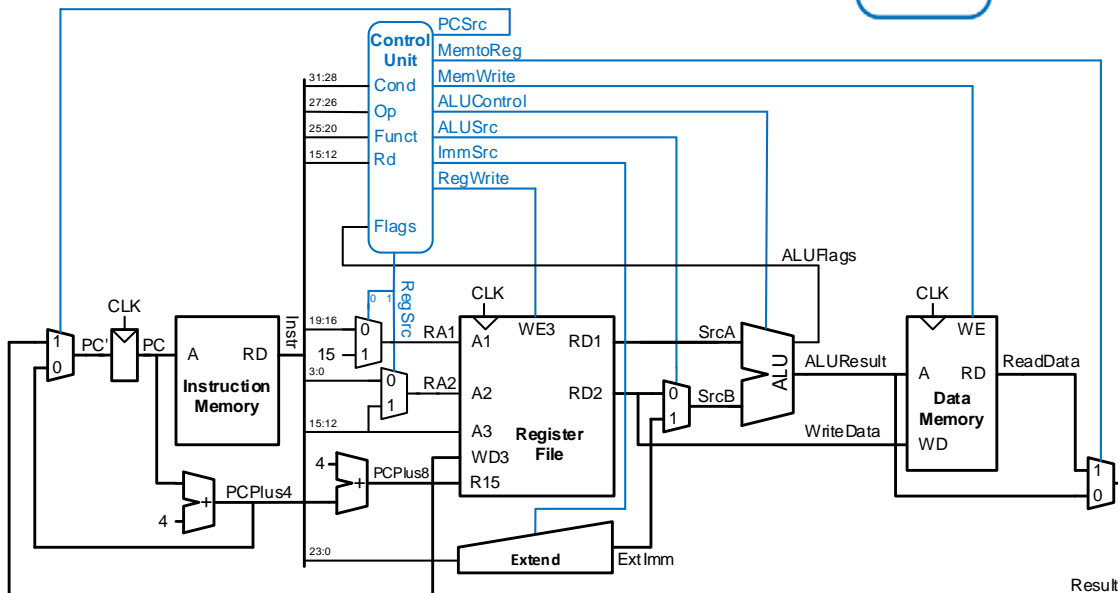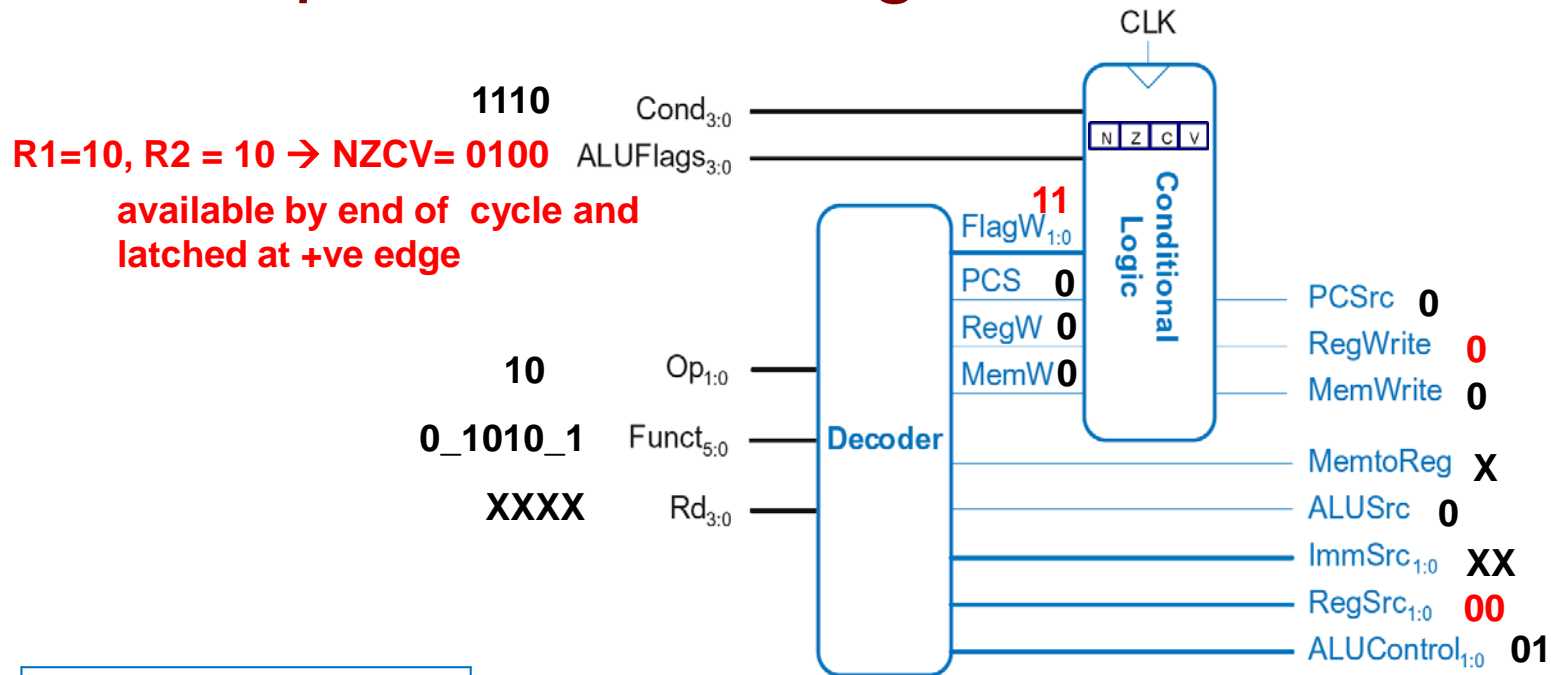
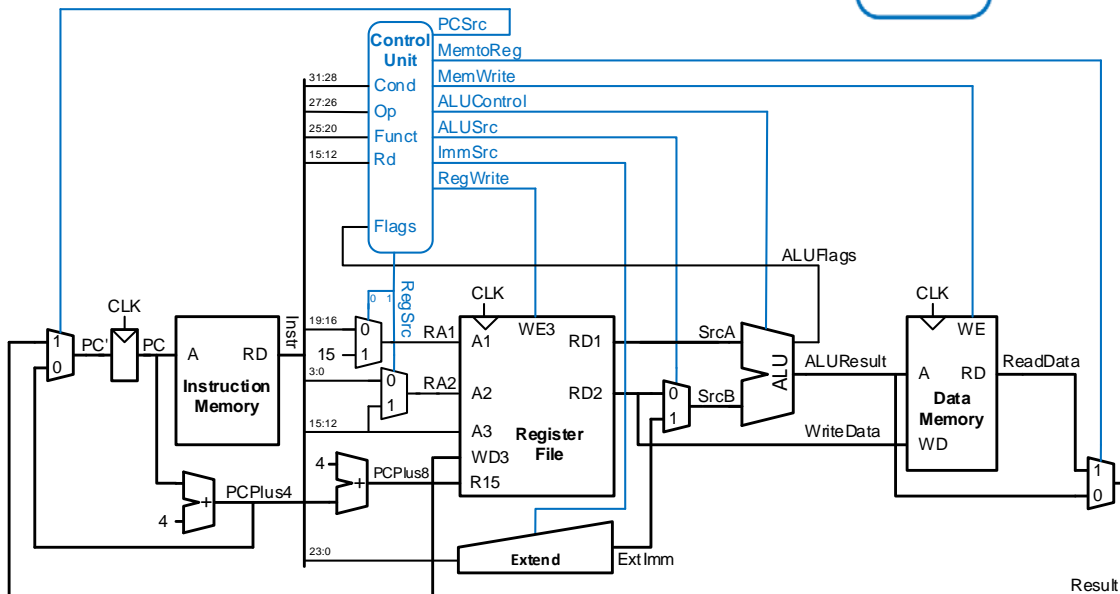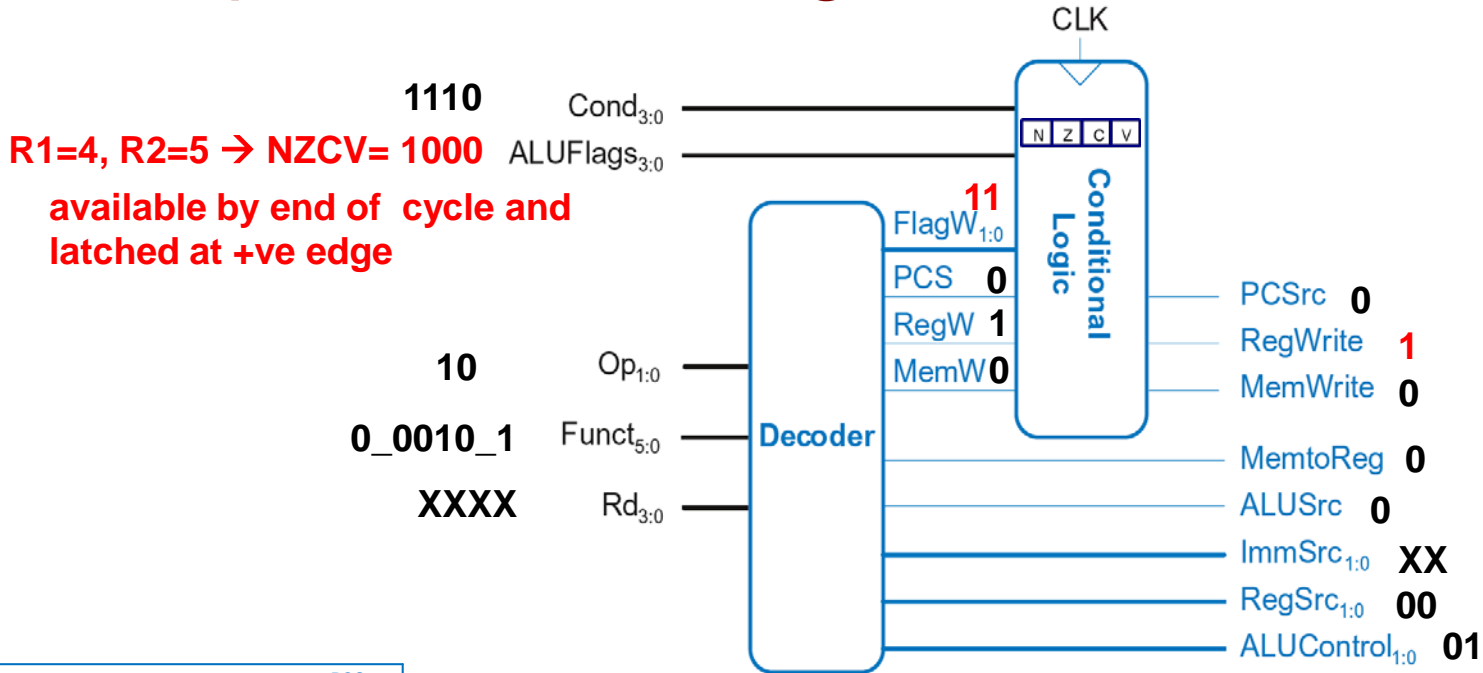
# Example of control logic: SUBS R3, R1, R2


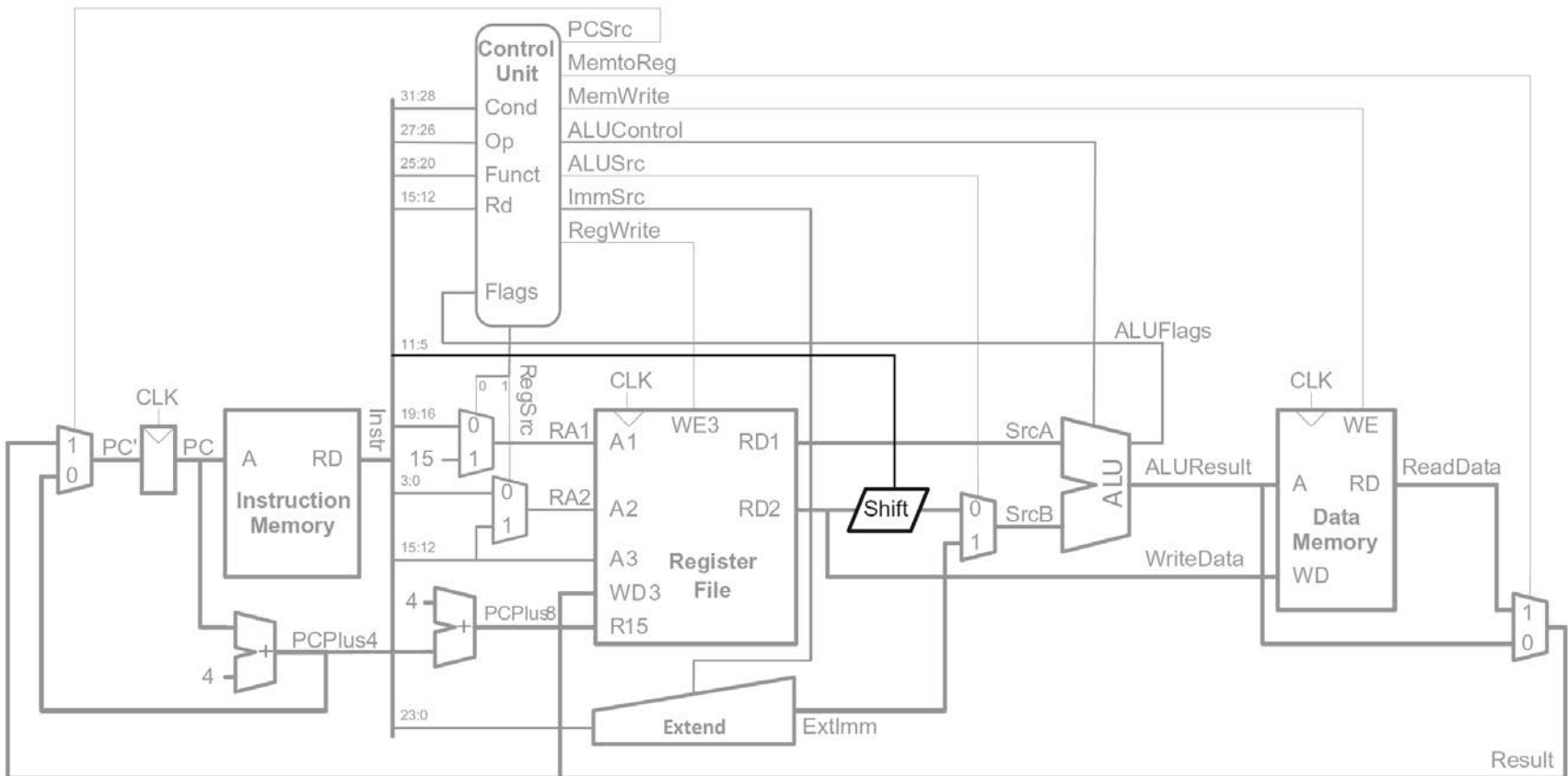
# Extended functionality: shifted register (by constant)



Assembly Code


Field Values

	31:28	27:26	25	24:21	20	19:16	15:12	11:7	6:5	4	3:0
ADD R7, R2, R12, LSR #5	14	0	0	4	0	2	7	5	0	1 <sub>2</sub> 0	12
	cond	op	l	cmd	S	rn	rd	shamt5	sh		rm

**No change to controller**
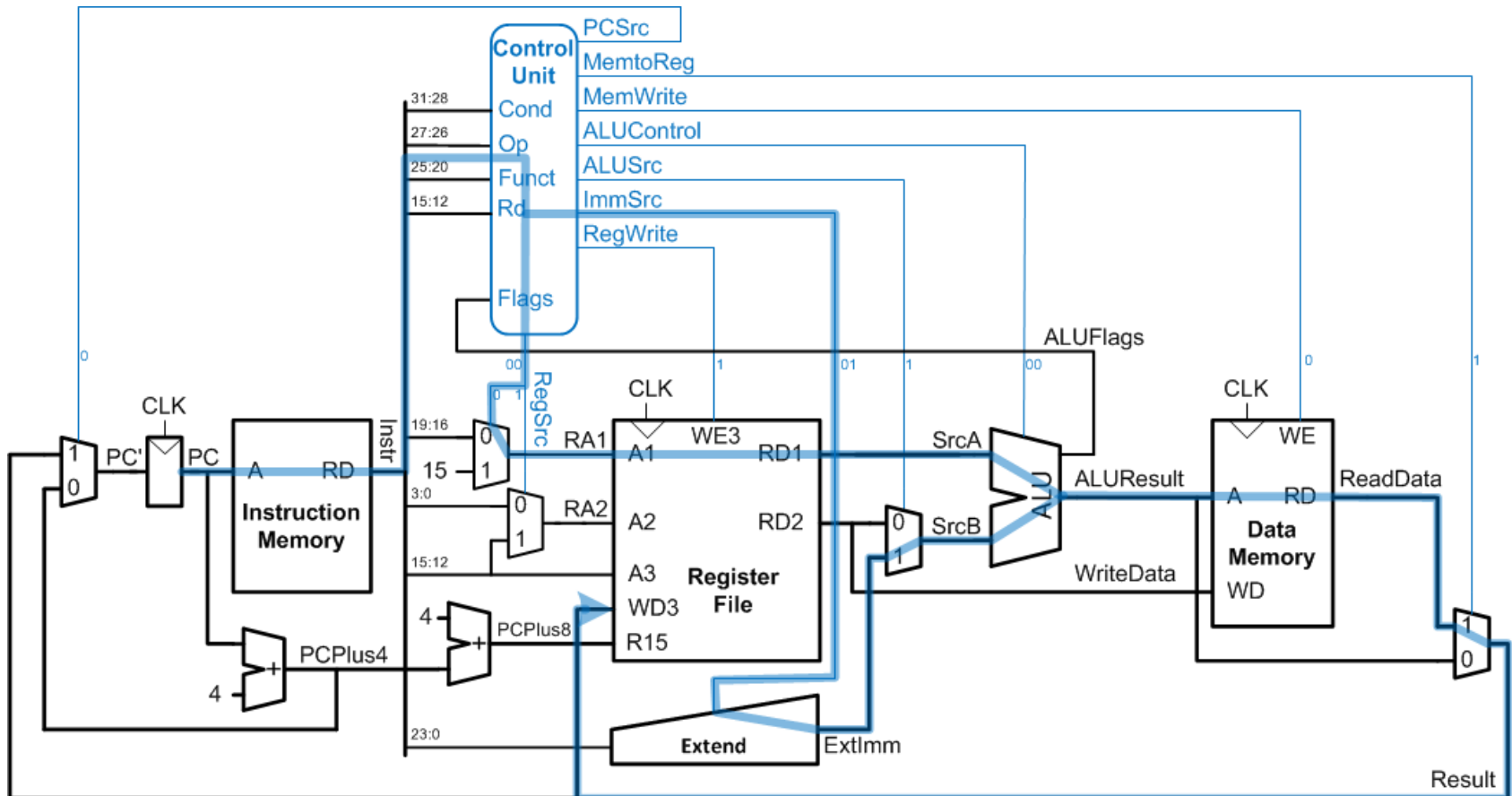
# Critical path

- $T_C$  is limited by the critical path (LDR)



- Single-cycle critical path:

$$T_{cl} = t_{pcq\_PC} + t_{mem} + t_{dec} + \max[t_{mux} + t_{RFread}, t_{sext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

# Critical path delay

- Single-cycle critical path:

$$T_{cl} = t_{pcq\_PC} + t_{mem} + t_{dec} + \max[t_{mux} + t_{RFread}, t_{sext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- In most cases:

$$- T_{cl} = t_{pcq\_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup}$$

Element	Parameter	Delay (ps)
Register clock-to-Q	$t_{pcq\_PC}$	40
Register setup	$t_{setup}$	50
Multiplexer	$t_{mux}$	25
ALU	$t_{ALU}$	120
Decoder	$t_{dec}$	70
Memory read	$t_{mem}$	200
Register file read	$t_{RFread}$	100
Register file setup	$t_{RFsetup}$	60

$$\begin{aligned} T_{cl} &= t_{pcq\_PC} + 2t_{mem} + t_{dec} + t_{RFread} + t_{ALU} + 2t_{mux} + t_{RFsetup} \\ &= [50 + 2(200) + 70 + 100 + 120 + 2(25) + 60] \text{ ps} \\ &= 840 \text{ ps} \end{aligned}$$

# Summary

- Single-cycle processor design is simple
- Plenty of room for improvement:
  - Multi-cycle
  - Pipelining
  - Superscalar
- In Lab05 you will design, implement and boot your first processor!