


EN2911X: Reconfigurable Computing

Lecture 02: Programmable Logic Technology (1)

Prof. Sherief Reda
Division of Engineering, Brown University
Fall '09




FPGA architecture

 


Objective of this lecture: study organization of programmable logic blocks and interconnects

Block logic element

 

[Rose'04]

 

[Maxfield'04]


- How is the number of bits in a K-input table?
- How many Boolean functions can a K-input LUT implement?
- What is the best LUT size?

Example


[from J. Zambreno]

$$F = A_0 A_1 A_3 + A_1 A_2 \bar{A}_3 + \bar{A}_0 \bar{A}_1 \bar{A}_2$$


4-input LUT

 

3-input LUT

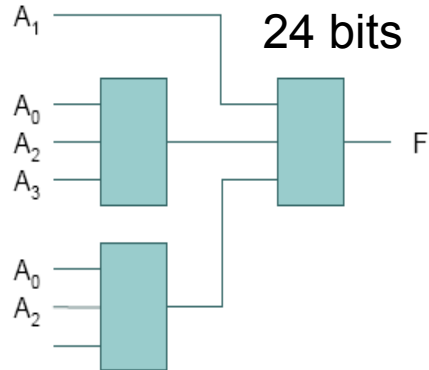


2-input LUT

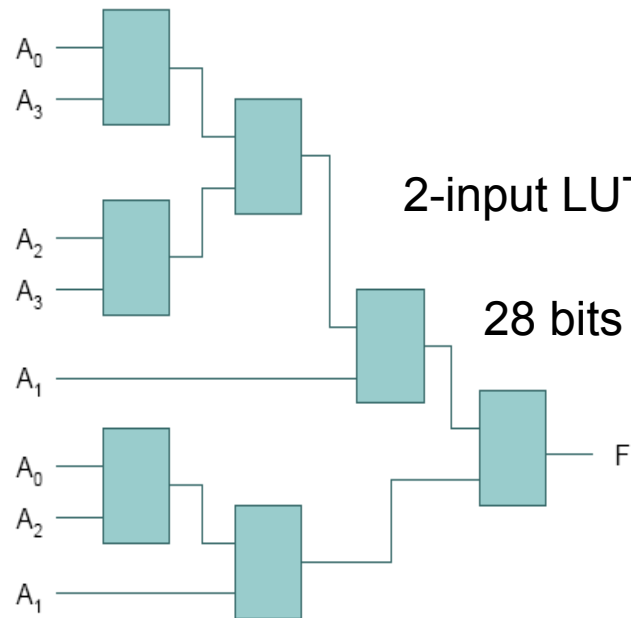


Logic block clusters (logic array block LAB, configurable logic block CLB)

 - Assume K -input LUT in each BLE and assume N BLEs per logic cluster
- The BLEs in each logic clusters are *fully connected* or “nearly-fully” connected
- What are the best values for I , K , and N ?



[Betz-Rose 97]

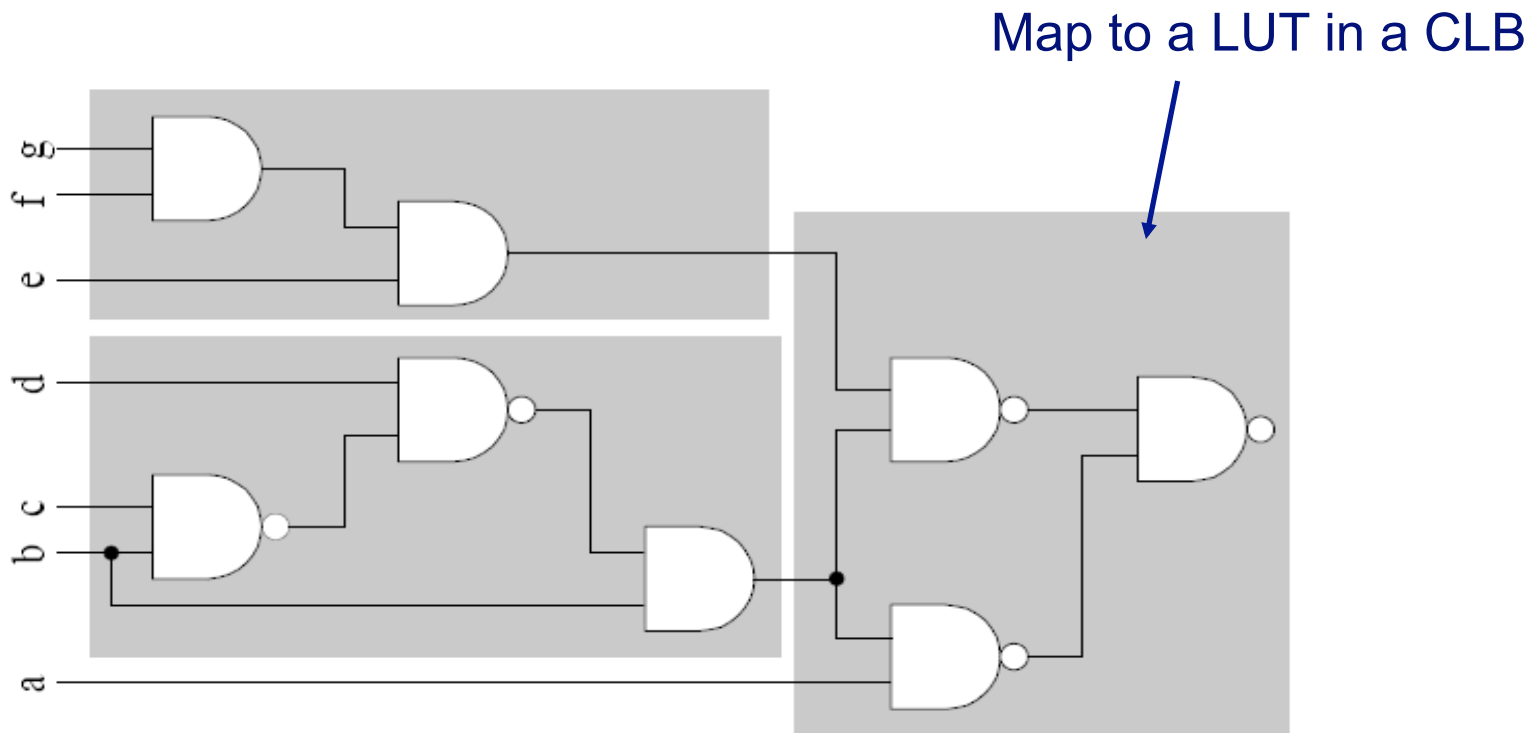To implement in FPGAs, designs need to be decomposed and mapped to LBs




[Figure from Cong FPGA'01]

Heterogeneous reconfigurable logic

- Reconfigurable fabric might contain non-reconfigurable elements that interface to the logic blocks through the programmable interconnect fabric
- Examples:
 - Embedded memory
 - Embedded multipliers, adders, MAC
 - Embedded processors

Embedded memory blocks


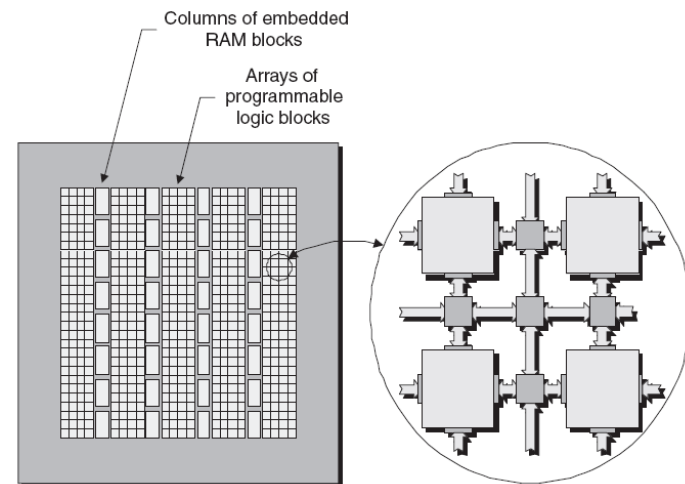
- Costly to implement memory with configurable logic blocks → add hard chunks of RAM blocks
- Position/size vary depending on the FPGA device. Size varies from few thousands (or tens of thousands) per RAM block
- Each block can be used independently or combined to form larger RAM blocks
- Could be single or dual-port RAMs



[Maxfield'04]


Embedded multipliers and adders

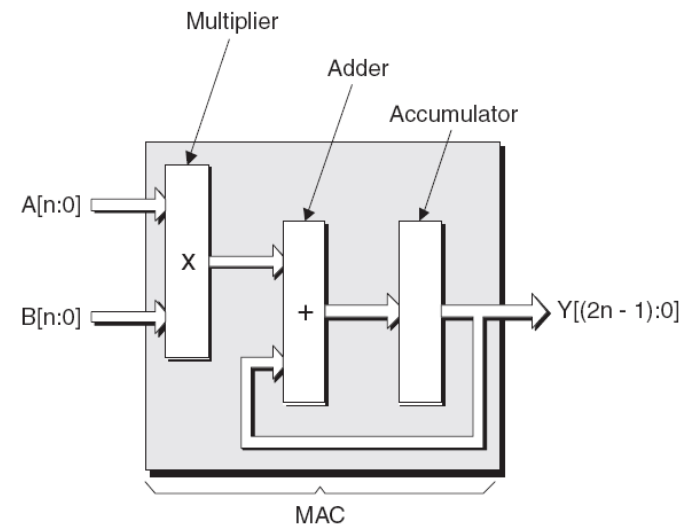 - Multipliers are inherently slow if implemented by connecting a large number of programmable logic blocks → add hard-wired multiplier blocks
- Typically located close to the embedded RAM blocks
- Some FPGA use Multiply-And-Accumulate (MAC) blocks (useful in DSP applications)




Programmable routing

 - Wires provide the necessary communication fabric to route the output of one computational node to the inputs of another computational node
- Why routing is very crucial?
 - Routing resources occupy a larger area than logic resources in an FPGA
 - Wire delay grows quadratically as a function of its length
 - Technology scaling reduces device delay but increases wire delay



General routing definitions

 

- A *wire segment* is a wire unbroken by programmable switches
- A *track* is a sequence of one or more wire segments in a line. The segments could be connected by switches at their ends
- A *routing channel* is a group of parallel tracks. The *channel width* is the number of tracks in the channel


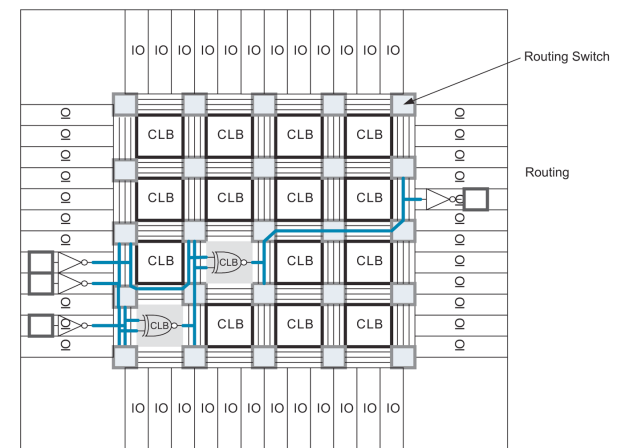




FIG 8.24 Personalized and routed FPGA

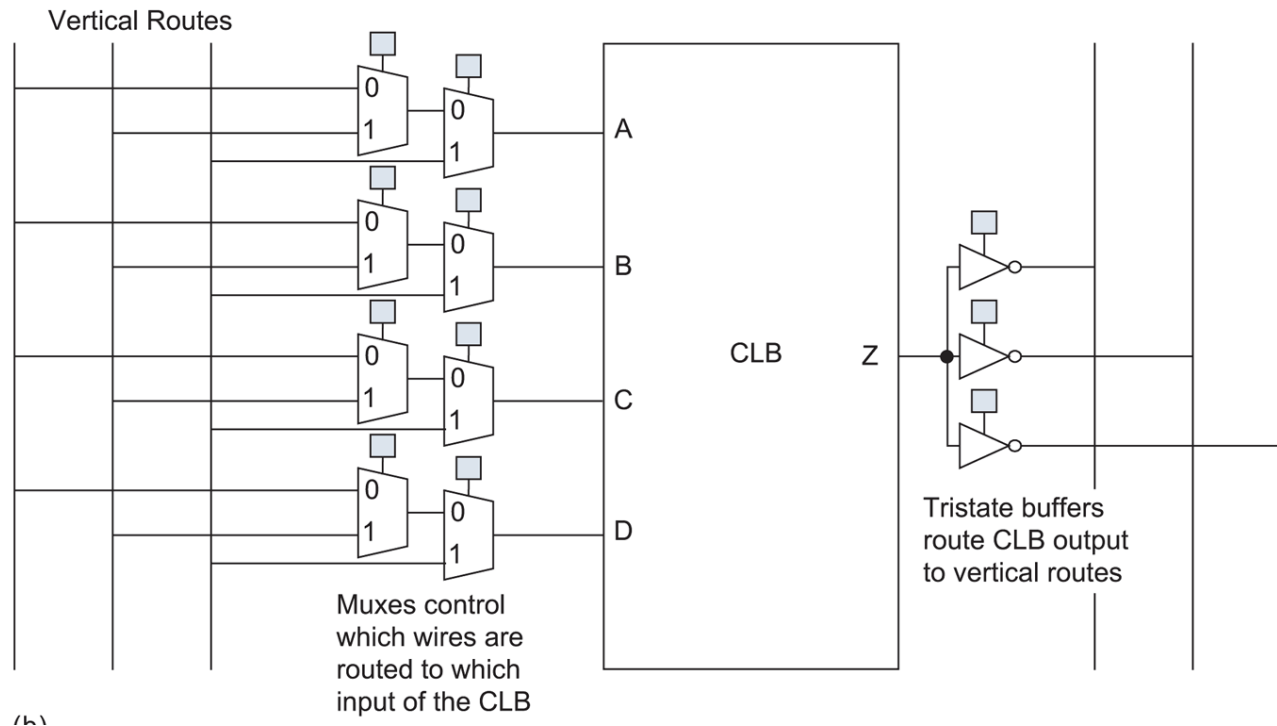Connection blocks: formed where CLB input or output pins connect to the routing channels




Life would have been easy if only logic blocks within the same column or row need to communicate!

  Segment-segment switch design for bidirectional wires




[Lemieux'04]

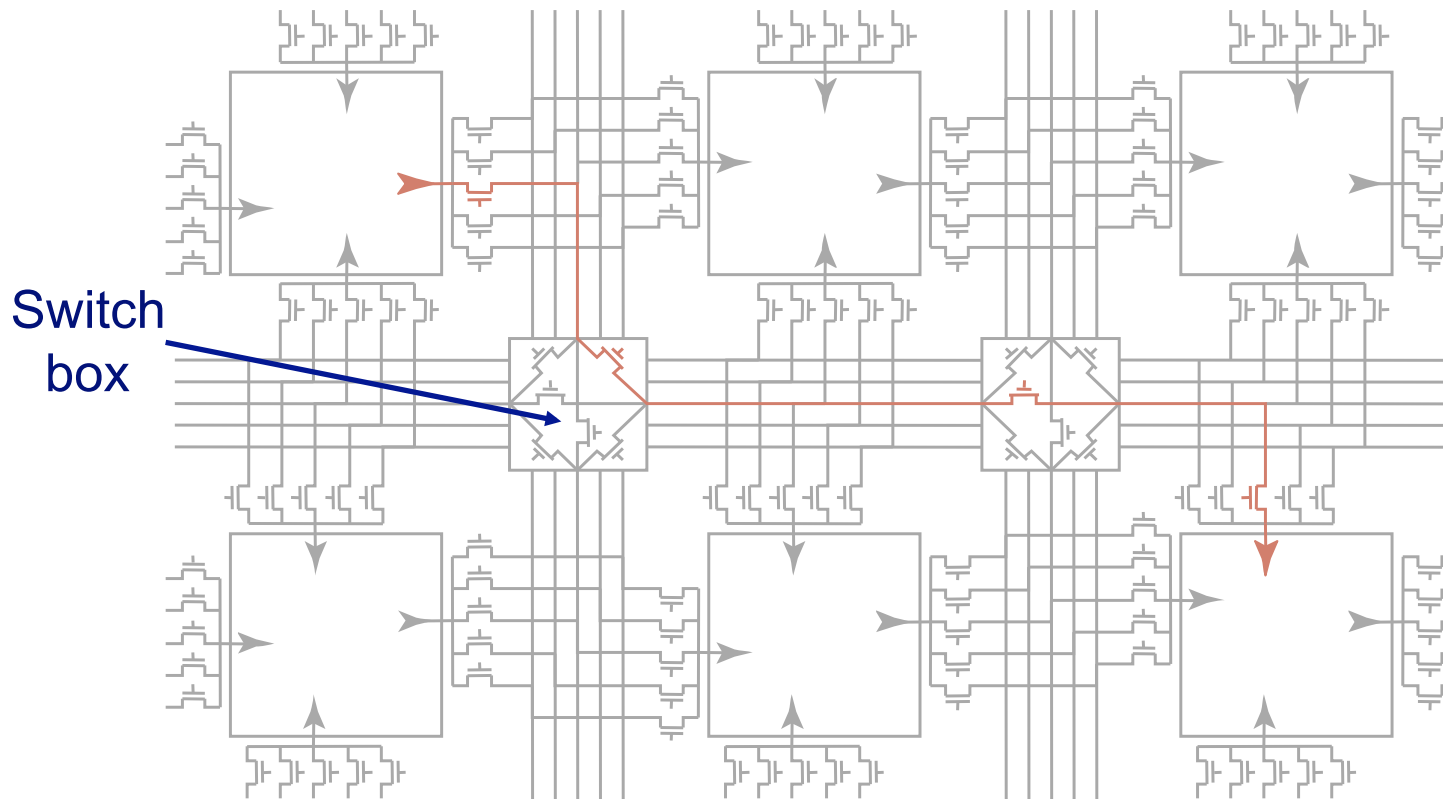Switch blocks: formed wherever horizontal and vertical channels intersect



Switch box size grows quadratically as a function of the number of its input wires


Bidirectional switch details

 

[Lemieux'04, Tessier]


Segmented and hierarchical routing

segmented routing

 

- Short wires accommodate local traffic
- Short wires can be connected together using switch boxes to emulate longer wires
- Also contain long wires to allow efficient communication without passing through switches


hierarchical routing

 

- Routing within a “group” of logic blocks occur at the local level
- Longer hierarchical wires connect different groups



Programming the FPGA

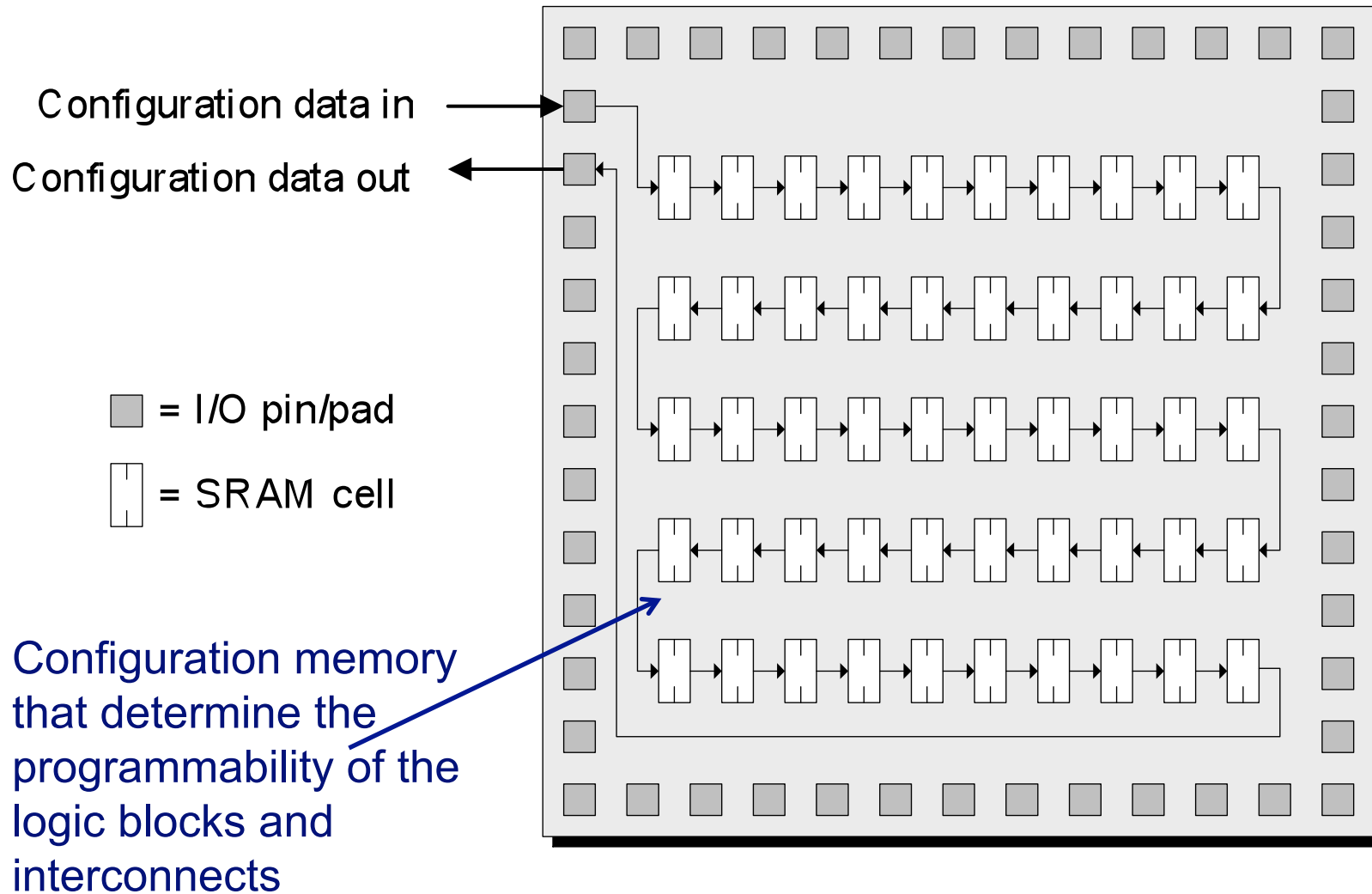

Programmable switch technology

Anti-fuse




Switch by default is OFF; when programmed it is ON.

Advantages:

- negligible delay
- small area overhead

Disadvantages:

 - not really reconfigurable; one time programmable



Flash



Switch by default is ON; when programmed it is OFF.

Advantages:

- programming not lost when device is turned off.

Disadvantages:

- requires more manufacturing steps

SRAM



SRAM bit cell stores the programmability of the device

Advantages:

- can be reconfigured quickly and as repeatedly as required
- no special fabrication steps

Disadvantages:

- takes more area
- loses charge when turned off



Assigned readings

- For Thursday Sept 17: Reconfigurable computing: A survey of systems and software. K. Compton & S. Huack (Sections 1-3)
- You have to submit a 1 (or more) page summary of the paper (main ideas + critique) before noon of the lecture day. Only use the submission form on the class website. Any summaries submitted after that time will not be looked at!