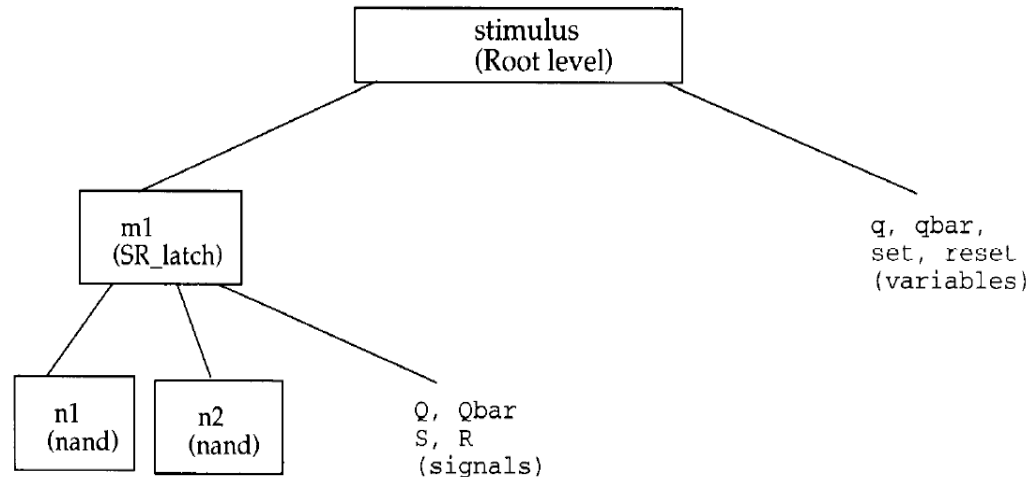


# EN2911X: Reconfigurable Computing

## Lecture 07: Verilog (4)

Prof. Sherief Reda  
Division of Engineering, Brown University  
Fall '09  
<http://scale.engin.brown.edu>

# Hierarchical naming



- As described, every module instance, signal, or variable is identified with an identifier.
- Each identifier has a unique place in the design hierarchy.
- Hierarchical name referencing allows us to denote every identifier in the design hierarchy with a unique name.
- A hierarchical name is a list of identifiers separated by dots “.” for each level of hierarchy
- Examples: `stimulus.q`, `stimulus.m1.Q`, `stimulus.m1.n2`

# Named blocks

- Blocks can be given names
  - Local variables can be declared from the names block
  - Variables in a named block can be accessed by using hierarchical name referencing
  - Named blocks can be disabled

```
...
always
begin : block1
    integer i;
    i=1;
...
end
...
always
begin : block2
    integer j;
    j = block1.i^1;
end
```

# Tasks and functions


- Often it is required to implement the same functionality at many times in a behavioral design.
- Verilog provides tasks and functions to break up large behavioral code into smaller pieces.
- Tasks and functions are included in the design hierarchy. Like named blocks, tasks and functions can be addressed by means of hierarchical names.
- Tasks have `input`, `output` and `inout` arguments
- Functions have `input` arguments
- Tasks and functions are included in the design hierarchy. Like named blocks, tasks or functions can be addressed by means of hierarchical names

# Functions

- Functions are typically used for combinational modeling (use for conversions and commonly used calculations).
- Need at least one input argument but cannot have output or inout arguments.
- The function is invoked by specifying function name and input arguments, and at the end execution, the return value is placed where the function was invoked
- Functions cannot invoke other tasks; they can only invoke other functions. Recursive functions are not synthesizable

```
module ...  
...  
reg [31:0] parity;  
  
always @(addr)  
begin  
    parity = calc_parity(addr);  
end  
  
// you can declare C style  
function calc_parity;  
input [31:0] address;  
begin  
    calc_parity = ^address;  
end  
endfunction  
...  
endmodule
```

# Sequential circuit design

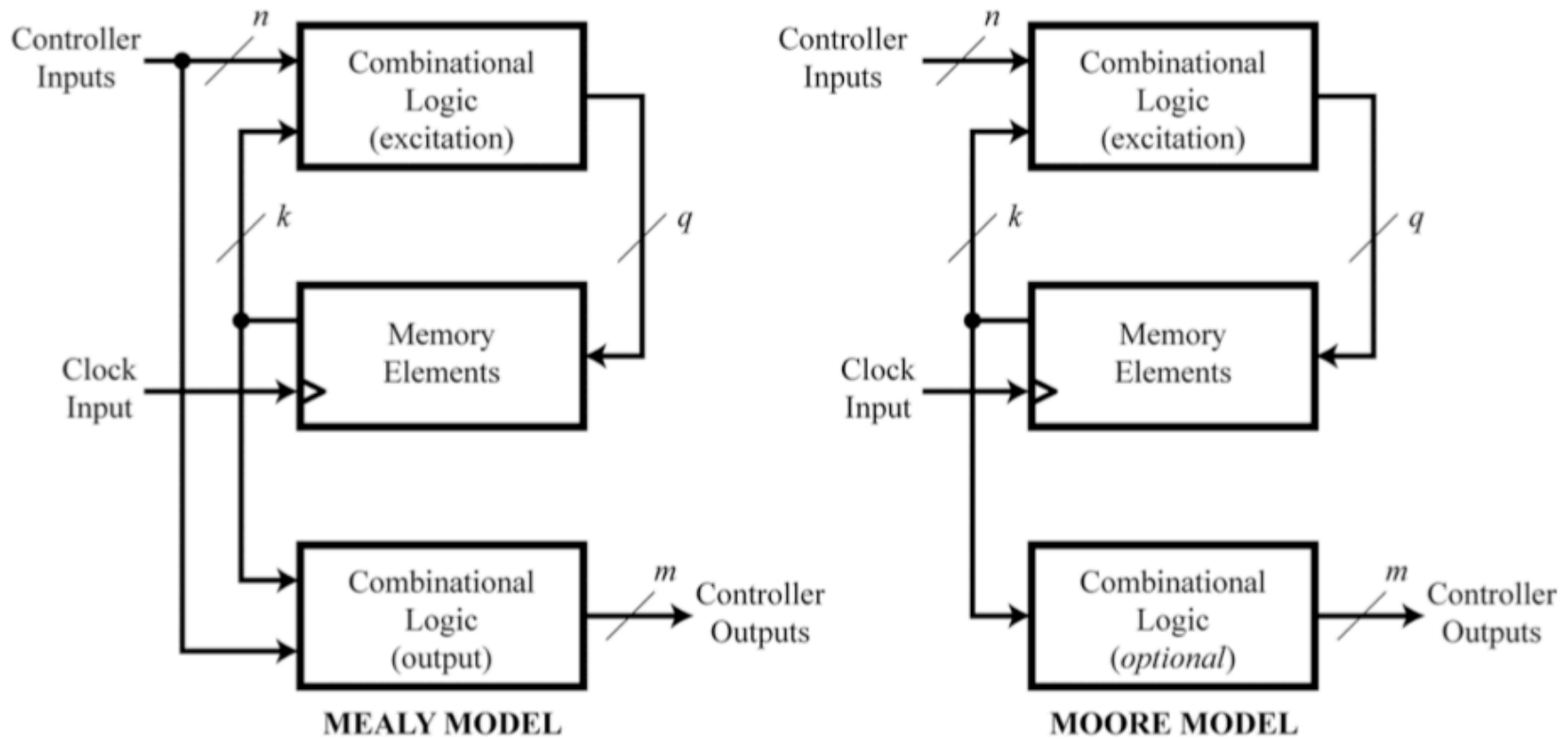


# Finite state machines (FSM) in Verilog




- Traffic signal for main highway gets highest priority, i.e., it is green by default.
- When cars from country road arrive at the intersection, the country traffic load should turn green after main highway turn yellow and then red.
- As soon as there are no cars on country road, country road should turn to yellow and then red.
- A car sensor (X) outputs 1 when there is a car waiting at country road; otherwise X outputs 0
- The two traffic signals can never be both green or yellow.

# State diagram

 



# Hardware organization

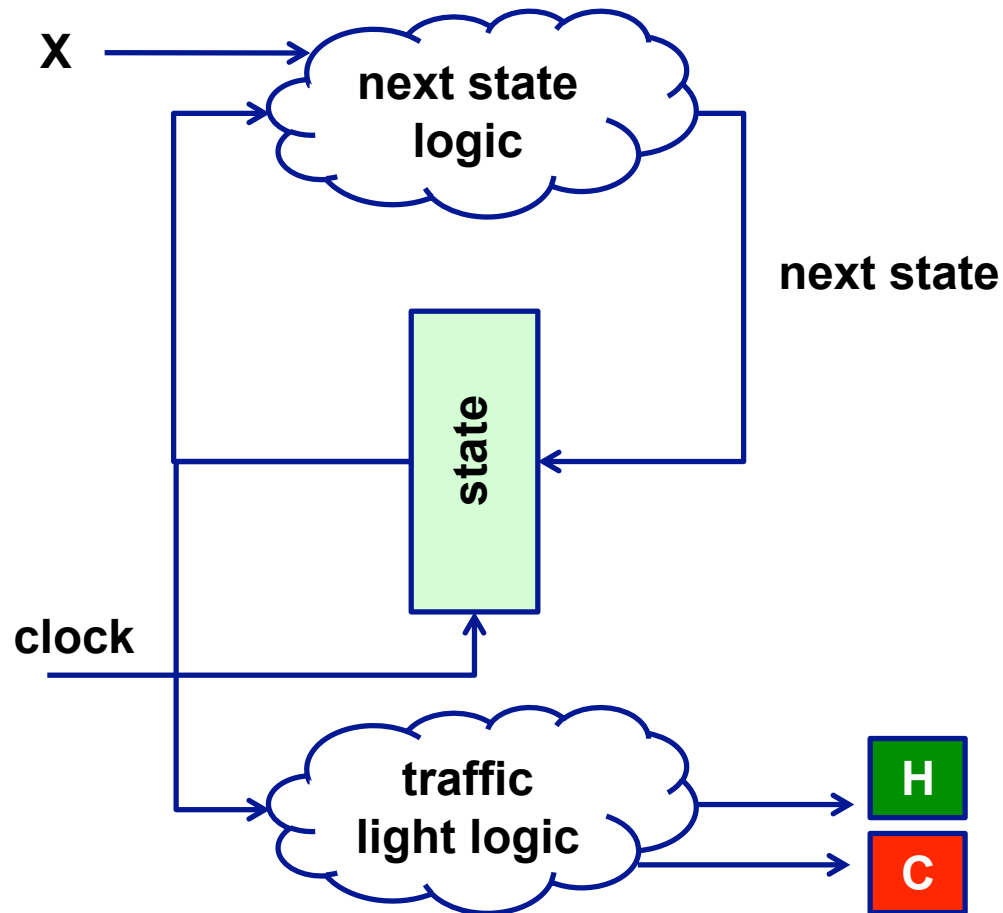

# Module definition

```
module traffic(hwy, cntry, X, CLOCK_50, clear);

output reg [1:0] hwy, cntry;
input X, CLOCK_50, clear;

reg [2:0] state, next_state;
integer count, ticks, last_tick;

parameter RED = 2'b01, YELLOW = 2'b10, GREEN = 2'b11;
parameter S0 = 3'd0, S1 = 3'd1, S2 = 3'd2, S3 = 3'd3, S4 = 3'd4;

initial
begin
    ticks = 0;
    count = 0;
    state = S0;
    next_state = S0;
end
.
.
.
end
```



# always statements inside the module

```
always @(posedge CLOCK_50)
    if (!clear) state <= S0;
    else state <= next_state;
```

```
always @(posedge CLOCK_50)
begin
    count <= count + 1;
    if (count == 50_000_000)
    begin
        count <= 0;
        ticks <= ticks +1;
    end
end
end
```

# always statements inside the module

```
always @(state)
begin
    hwy = GREEN;
    cntry = RED;
    case(state)
        S0: ;
        S1: hwy = YELLOW;
        S2: hwy = RED;
        S3: begin
            hwy = RED;
            cntry = GREEN;
        end
        S4: begin
            hwy = RED;
            cntry = YELLOW;
        end
    endcase
end
```

# always statements inside the module

```
always @(state or X)
begin
    case (state)
    S0: if(X == 1'b1)
    begin
        next_state = S1;
        last_tick = ticks;

    end
    else next_state = S0;
    S1: begin
        if (ticks == last_tick+2) next_state = S2;
        else next_state = S1;

    end
    S2: begin
        if (ticks == last_tick+2) next_state = S3;
        else next_state = S2;

    end
    S3: if(X)
    begin
        next_state = S3;
        last_tick = ticks;

    end
    else next_state = S4;
    S4: begin
        if (ticks == last_tick+2) next_state = S0;
        else next_state = S4;

    end
    default: next_state = S0;
    endcase
end
```

